



Chapter 9: Electronic Building Blocks



What's a Microcontroller?



Presentation based on:
"What's a Microcontroller ?"
By Andy Lindsay
Parallax, Inc

Presentation developed by:
Martin A. Hebel
Southern Illinois University Carbondale
College of Applied Sciences and Arts
Electronic Systems Technologies

10/26/03





Presentation Index

What's a Microcontroller?

- ✓ [Use and Copyright](#)
- ✓ [Those Little Black Chips](#)
- ✓ [ACTIVITY #1: Control Current With Transistor](#)
- ✓ [ACTIVITY #2: Digital Potentiometer](#)
- ✓ [Review Questions](#)
- ✓ [Links](#)



Use and Copyright

What's a Microcontroller?

This presentation supplements "**What's a Microcontroller**" by Andy Lindsay. ([Link to text](#) at Parallax)

- ✓ This presentation is not a replacement for the text.
- ✓ Important concepts of the text are highlighted.
- ✓ In some cases, additional material has been added to augment the text. Denoted by titles colored **gold**.
- ✓ Full program listings are generally not provided in the presentation.

Distribution:

This presentation may be freely distributed without modifications. Modifications are permitted by schools and organizations for internal use only. Credits, use and copyright slides must remain.



COPYRIGHTS AND TRADEMARKS

This documentation is Copyright 2003 by Parallax, Inc. By downloading or obtaining a printed copy of this documentation or software you agree that it is to be used exclusively with Parallax products. Any other uses are not permitted and may represent a violation of Parallax copyrights, legally punishable according to Federal copyright or intellectual property laws. Any duplication of this documentation for commercial uses is expressly prohibited by Parallax, Inc. Check with Parallax for approval prior to duplicating any of our documentation in part or whole for any use.

BASIC Stamp is a registered trademark of Parallax, Inc. If you decide to use the name BASIC Stamp on your web page or in printed material, you must state that "BASIC Stamp is a registered trademark of Parallax, Inc." Other brand and product names are trademarks or registered trademarks of their respective holders.

DISCLAIMER OF LIABILITY


Parallax, Inc. and Southern Illinois University are not responsible for special, incidental, or consequential damages resulting from any breach of warranty, or under any legal theory, including lost profits, downtime, goodwill, damage to or replacement of equipment or property, or any costs of recovering, reprogramming, or reproducing any data stored in or used with Parallax products. Parallax is also not responsible for any personal damage, including that to life and health, resulting from use of any of our products. You take full responsibility for your BASIC Stamp application, no matter how life threatening it may be.



Those Little Black Chips

What's a Microcontroller?

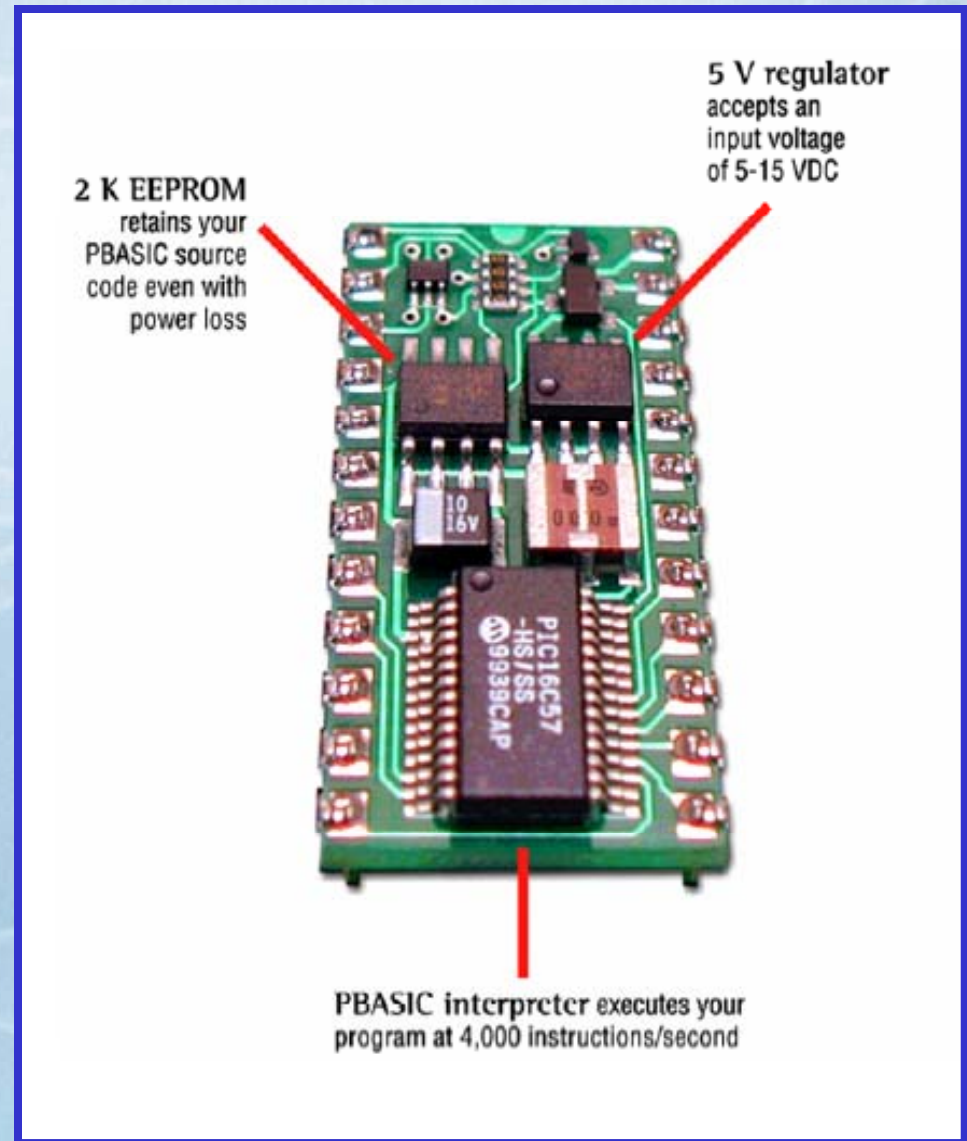The BASIC Stamp itself has many examples of "little black chips" which perform specific functions.





What's a Microcontroller?

An Integrated Circuit (IC) is the term used for the little black chips.

Inside the black plastic or ceramic case is a tiny silicon chip which hundreds or thousands of transistors.

The transistor is the basic building block of integrated circuits, but may be used individually also.

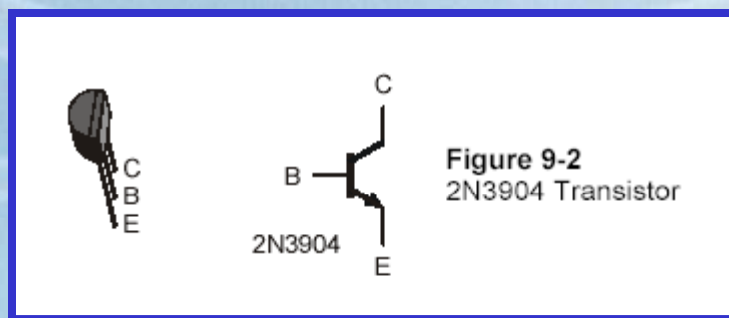


Figure 9-2
2N3904 Transistor




ACTIVITY #1: Control Current With Transistor

What's a Microcontroller?

- A transistor is a current controlled device.
- ✓ Current on the Base-Emitter will control the Collect-Emmitter current flow with amplification.
 - ✓ The amplification factor, called Beta or h_{FE} , is typically a value of 100, though may be much higher such as 416.
 - ✓ $I_{CE} = I_{BE} \times h_{FE} = 1\text{mA} \times 416 = 416\text{mA}$.

Control Current = 1mA

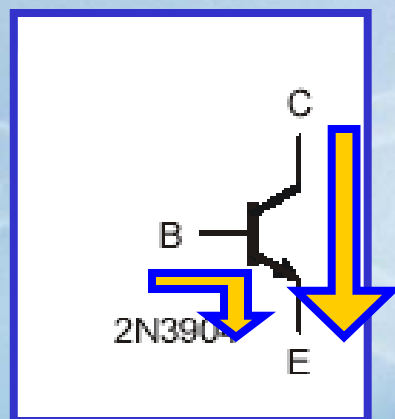

Drive current = 416 mA



What's a Microcontroller?

In the activity, the potentiometer is used to adjust voltage, and thus current, into the base of transistor.

As the potentiometer is adjusted, the base current will change adjusting the emitter current to the LED.

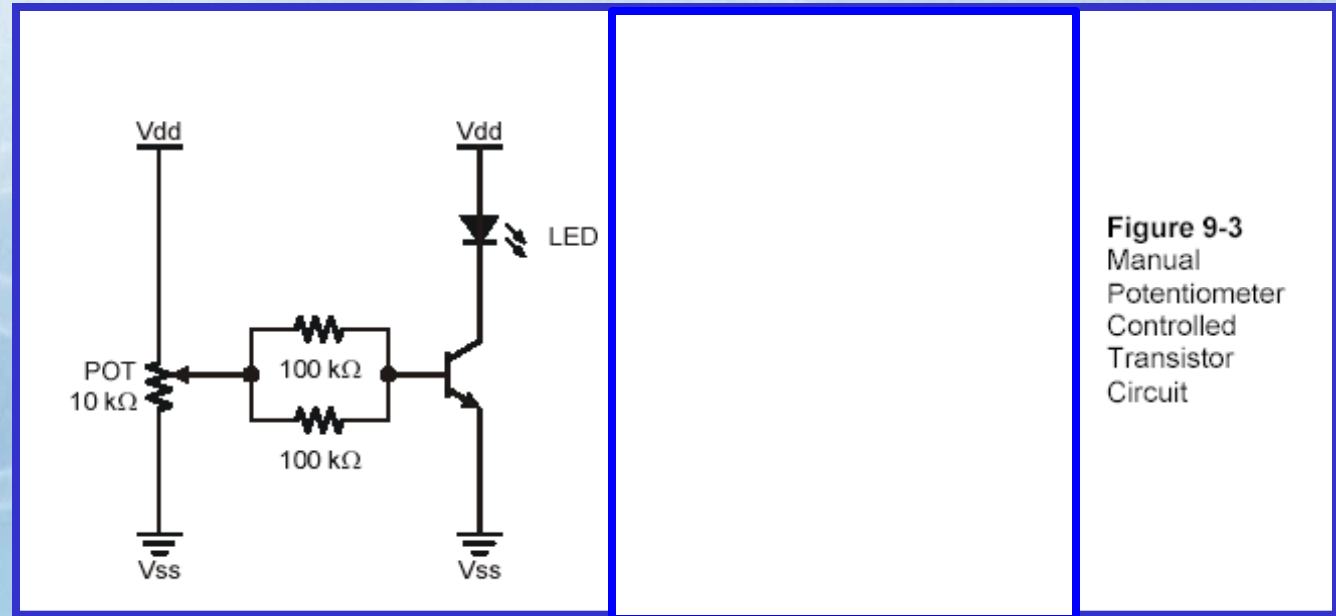


Figure 9-3
Manual
Potentiometer
Controlled
Transistor
Circuit



What's a Microcontroller?

If the potentiometer is adjusted to 2.5V, minus 0.7 lost at the base-emitted junction, provides:
 $(2.5V - 0.7V) / 50K = 36\mu A$.

This will provide current to LED at a value of:
 $36\mu A \times 416 = 15mA$.

What would be the current to the LED if potentiometer is adjusted to 3.0V?



ACTIVITY #2: Digital Potentiometer

What's a Microcontroller?

The Digital Potentiometer acts the same as a standard potentiometer by adjusting the wiper to change the resistance above and below the tap to adjust the voltage at the wiper.


In this case though the tap is digitally controlled by opening and closing 1 of 128 possible switches (really transistors).



What's a Microcontroller?

Each element is 78.125 ohms, and with 128 of them, 10K ohm total.

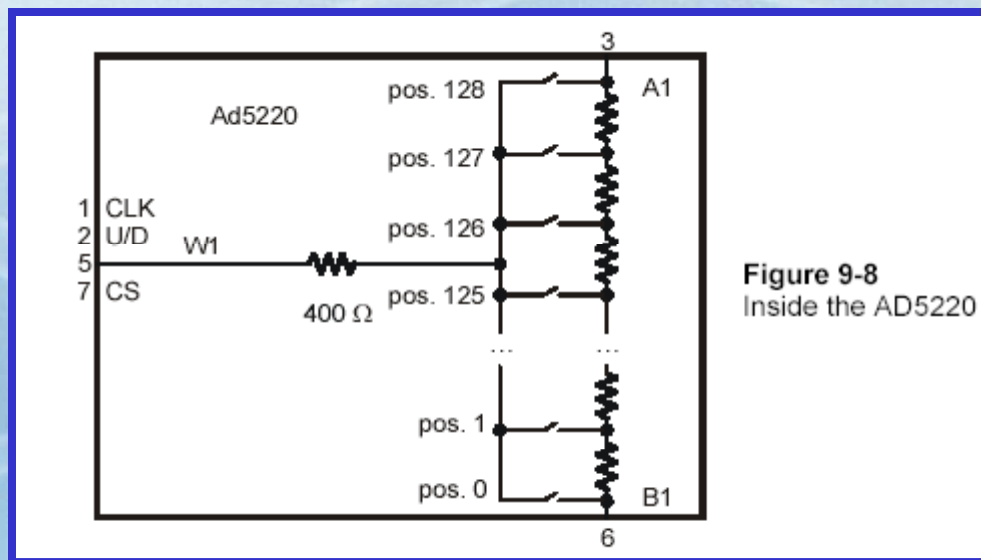With anyone tap closed, the 10K ohm resistance will be split and the voltage at the tap will be varied.





What's a Microcontroller?

Control lines are used to shift the active tap up or down to change the voltage at the wiper.

CS - Chip Select – Must be LOW to modify the chips tap.

CLK – Clock – Each pulse on CLK will move the tap position.

U/D – Defines the direction to move the tap.

1 = Up towards A1

0 = Down towards B1.



What's a Microcontroller?

By setting the direction and clocking, the tap will be moved.

```
' What's a Microcontroller - DigitalPotUpDownWithToggle.bs2
' Sweep digital pot through values.
' {$STAMP BS2}
' {$PBASIC 2.0}
counter VAR Byte
LOW 5
DO
  FOR counter = 0 TO 128
    PULSOUT 6,5
    PAUSE 10
  NEXT
  TOGGLE 5
LOOP
```

Set Direction
Low for Down to B1

Pulse clock to move tap
128 times

Reverse direction
and repeat

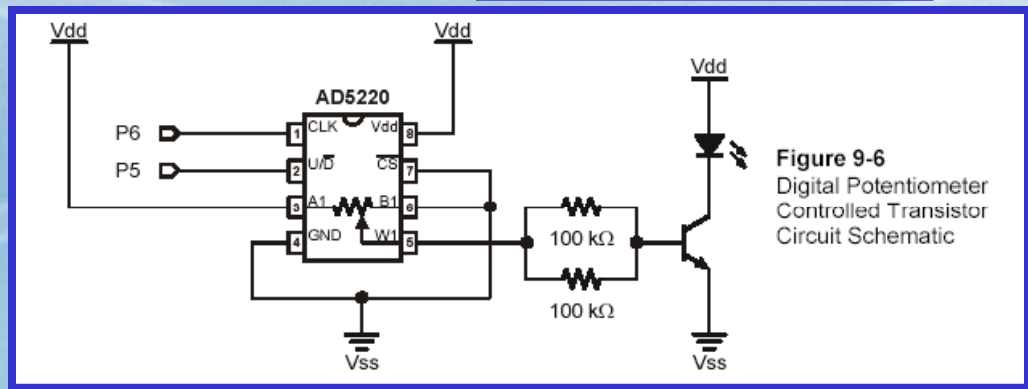


Figure 9-6
Digital Potentiometer
Controlled Transistor
Circuit Schematic



Review Questions

What's a Microcontroller?

- ✓ IC is short for **Integrated Circuit**.
- ✓ An IC is made with many many **Transistor**.
- ✓ With a transistor, the **Base** current controls the **Collector** current.
- ✓ The **CS** input on the digital potentiometer allows operation.
- ✓ The **U/D** line on the digital potentiometer controls the tap change direction.
- ✓ The **CLK** line on the digital potentiometer controls when to change the tap position.
- ✓ If at tap 90, and U/D is low, CLK is clocked 3 times, the new tap position will be **87**.



Links

What's a Microcontroller?

- ✓ [BASIC Stamp Home](#)
- ✓ [Stamps In Class Home](#)
- ✓ [BASIC Stamp Software](#)
- ✓ [BASIC Stamp Robots](#)
- ✓ [BASIC Stamp Yahoo Group](#)
- ✓ [Stamps In Class Yahoo Group](#)
- ✓ [SIUC EST Degree](#)