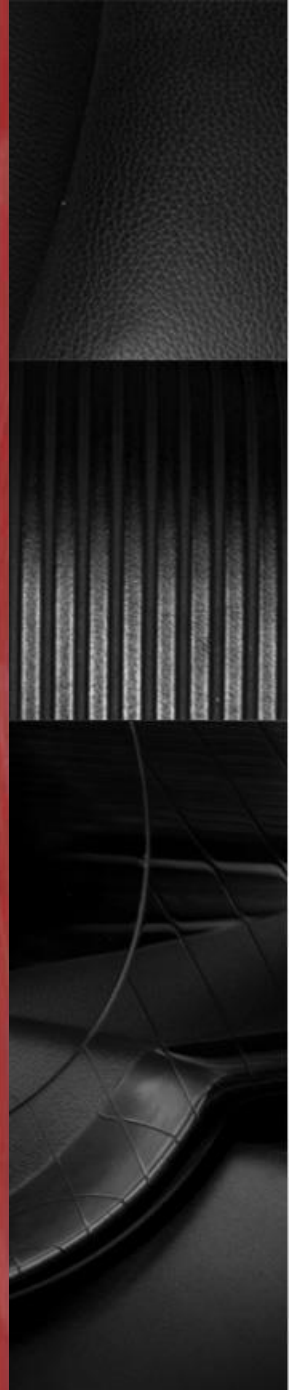


EECT 112 & Projects from MultiSim

Jeff Noggle & Stephen Smith

EECT 112

Summer 2013





Contents

- Conversion Table
- Multisim Circuits
- Boolean Diagrams using Multisim
- LABS
- Final Project





- Additional Data
 - Logic Gates, Boolean Diagrams, Chip Diagrams,

Using Multisim. . . It's a BLAST!!!!





Dual NAND Gates and Methods to set them up:



Slides 2 thru 5

  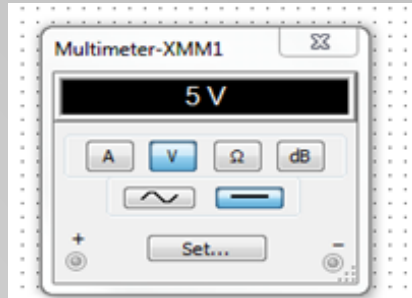 


NAND GATES – Setup one

 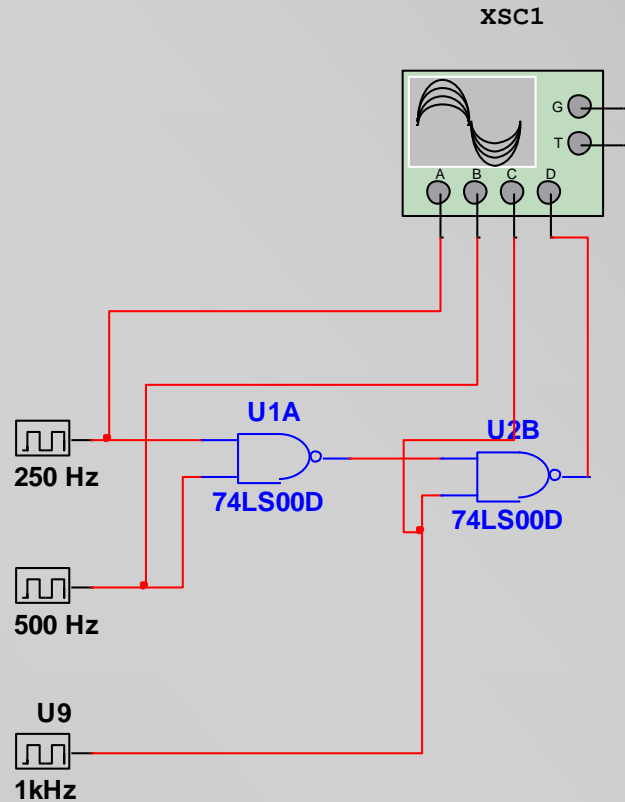


NAND GATES – Setup Two

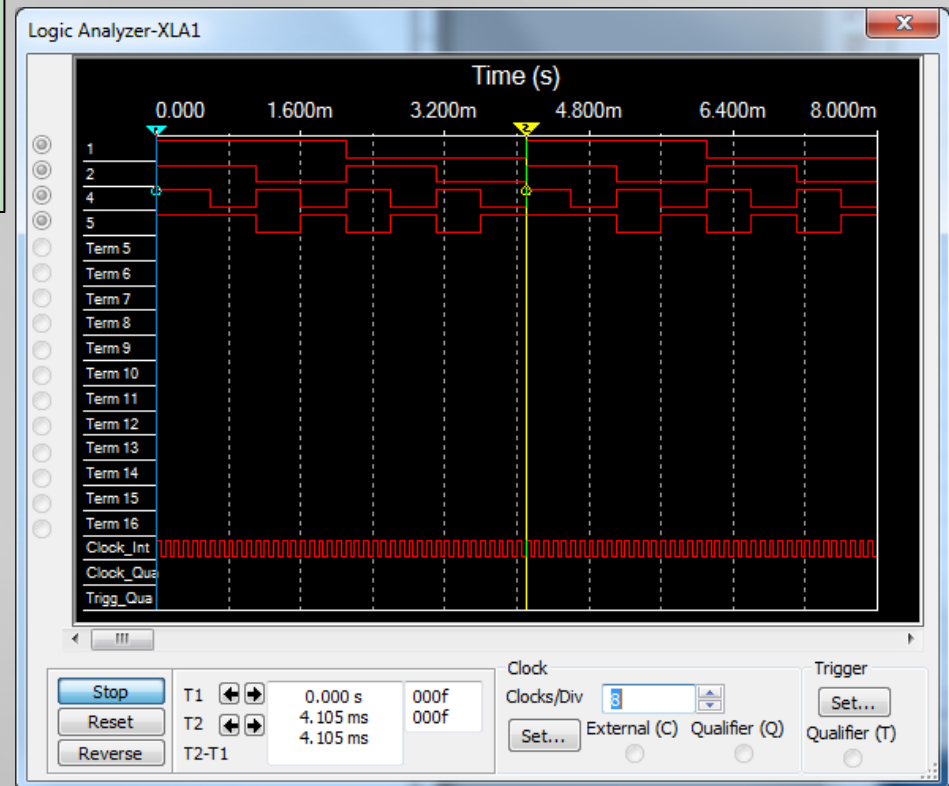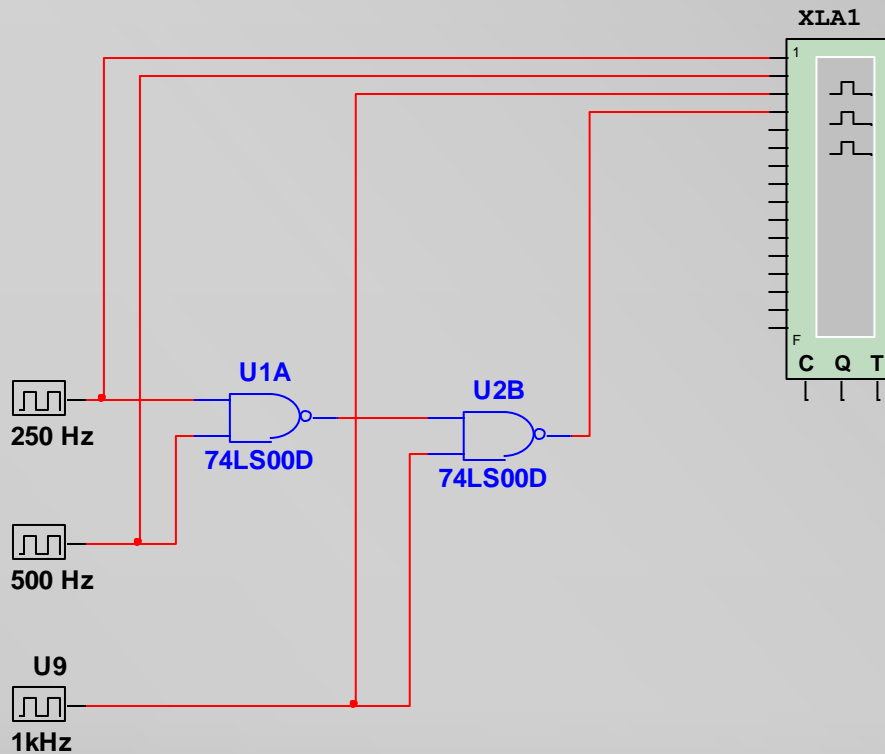


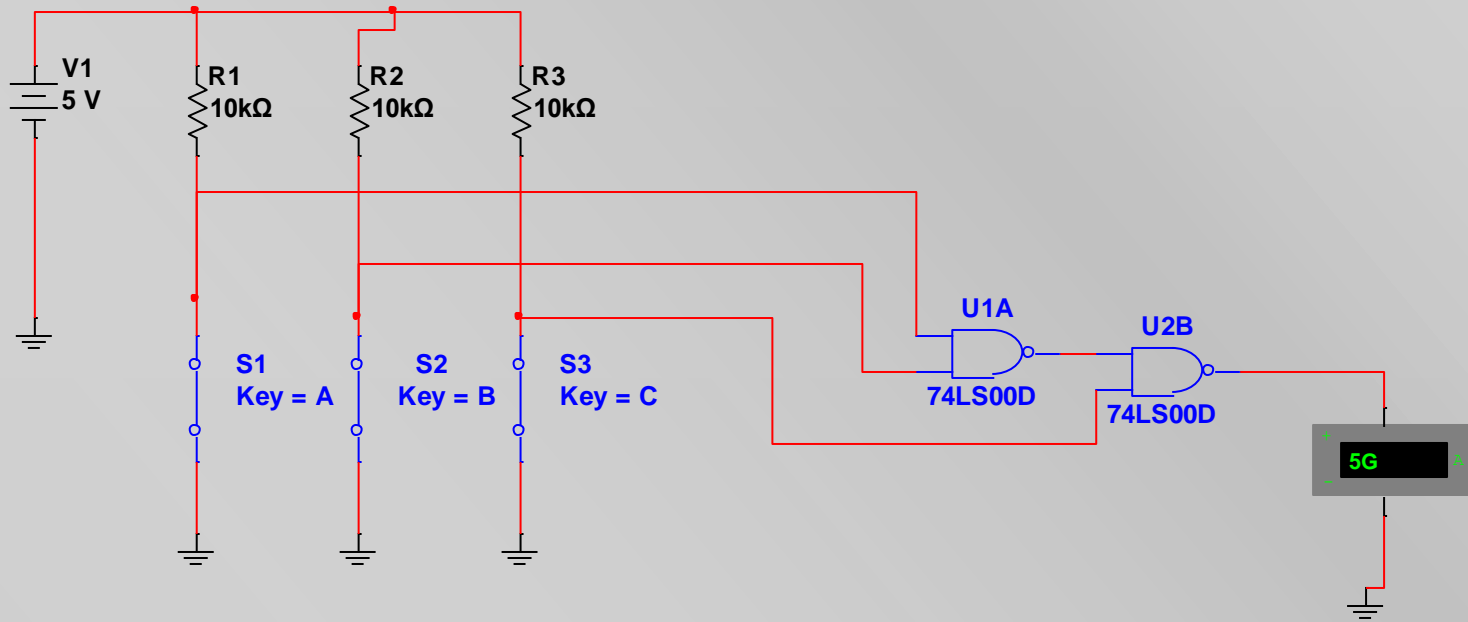

Boolean Theorems for AND Gates

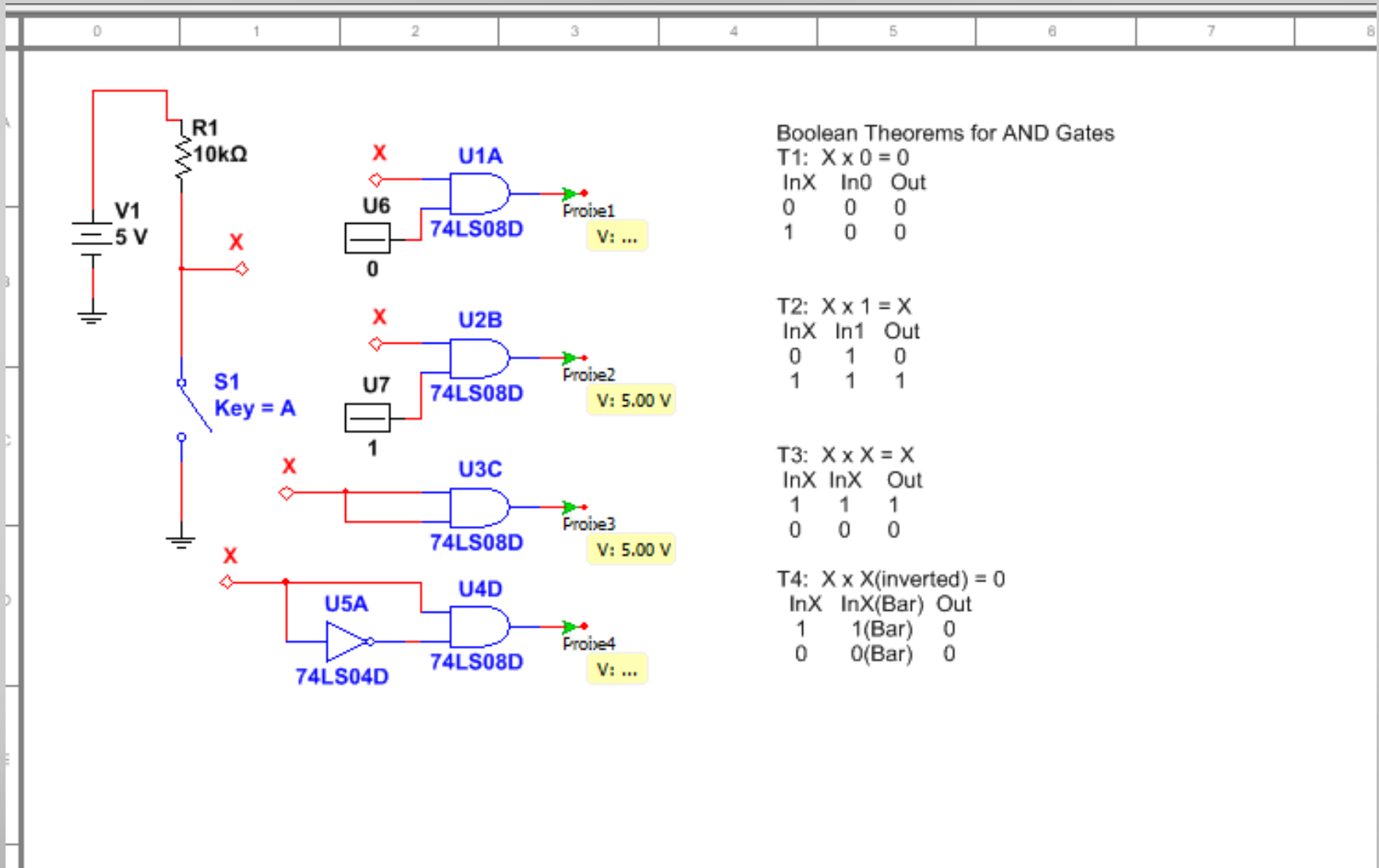

Boolean Theorems for OR Gates

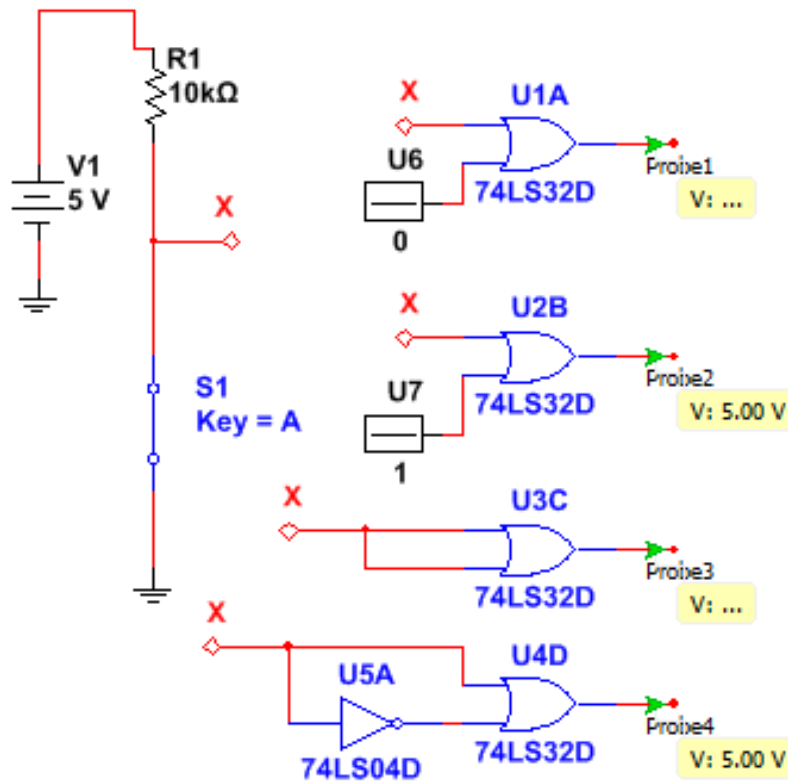

Boolean Theorems for OR Gates

T1: $X \times 0 = X$

InX	In0	Out
0	0	0
1	0	1

T2: $X \times 1 = 1$

InX	In1	Out
0	1	1
1	1	1


T3: $X \times X = X$

InX	InX	Out
1	1	1
0	0	0

T4: $X \times X(\text{inverted}) = 1$

InX	InX(Bar)	Out
1	1(Bar)	1
0	0(Bar)	1


Multivariable Distributive Laws 13a

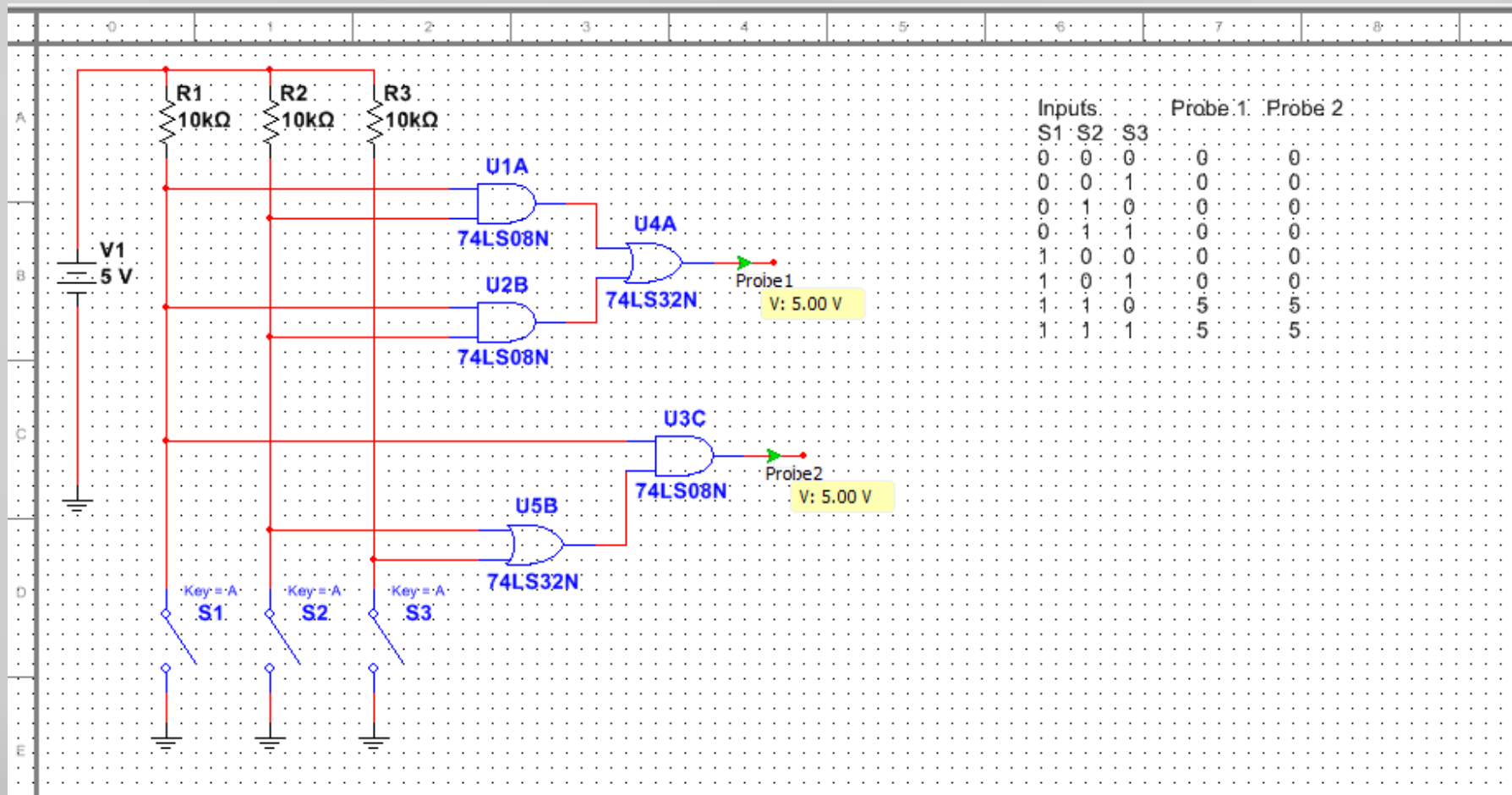

$$(13a) \quad x(y + z) = xy + xz$$

$$(13b) \quad (w + x)(y + z) = wy + xy + wz + xz$$


Multivariable Distributive Law 13b

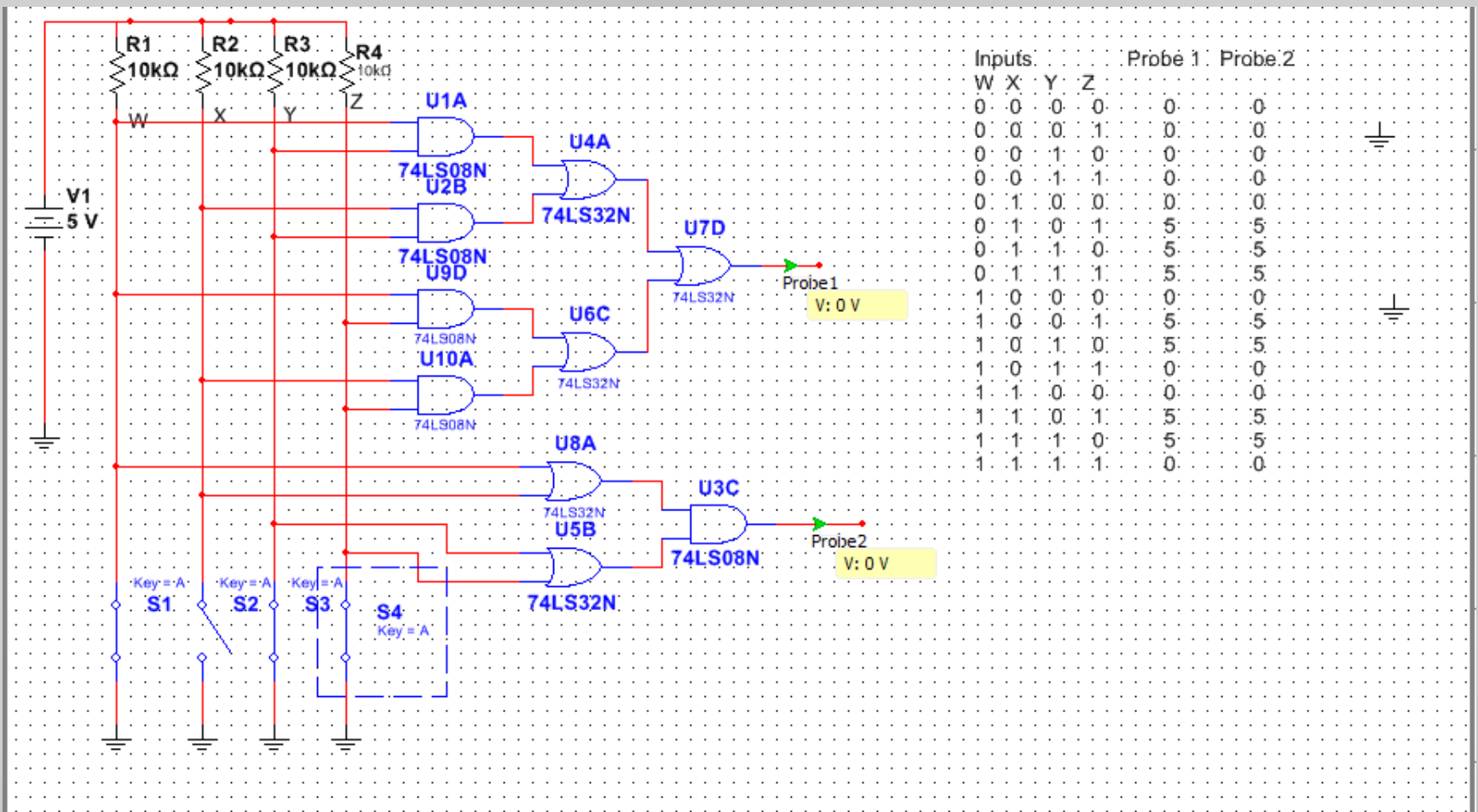

(13a) $x(y + z) = xy + xz$


(13b) $(w + x)(y + z) = wy + xy + wz + xz$

3 input OR Gate

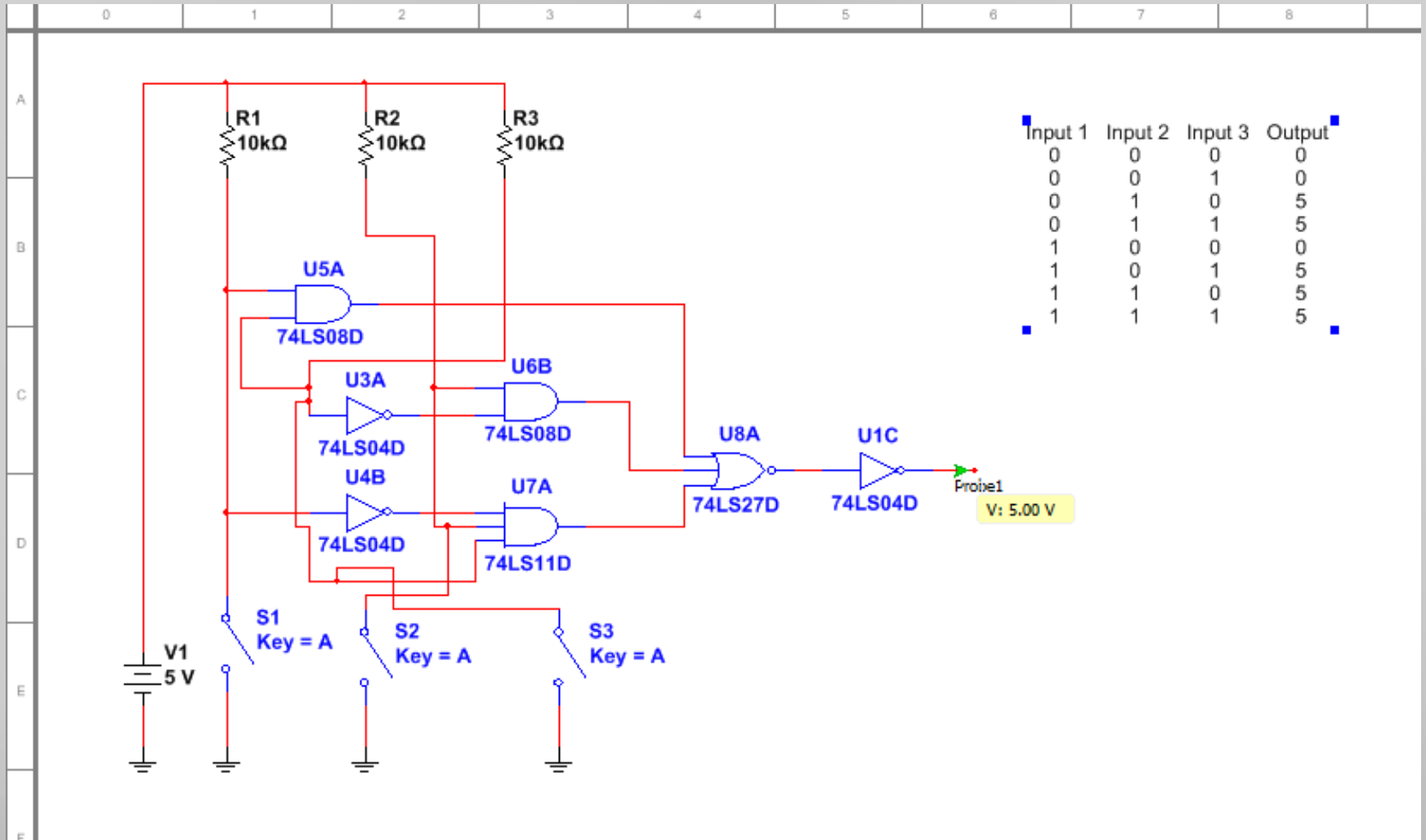


Lecture 3, Slide 20, Simulated on MultiSim


3 Input AND with Inverter Circuit

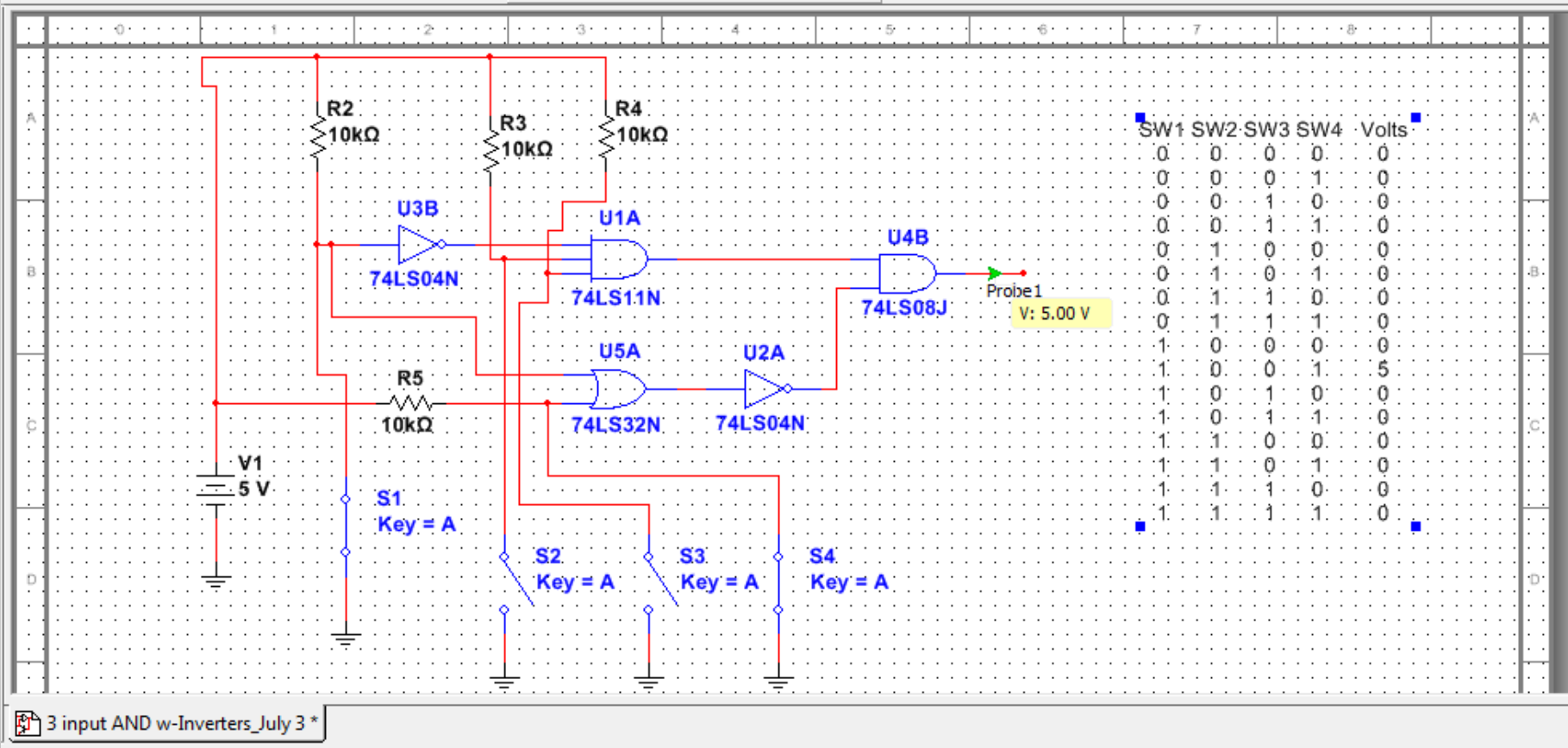


Universality of NAND and NOR Gates

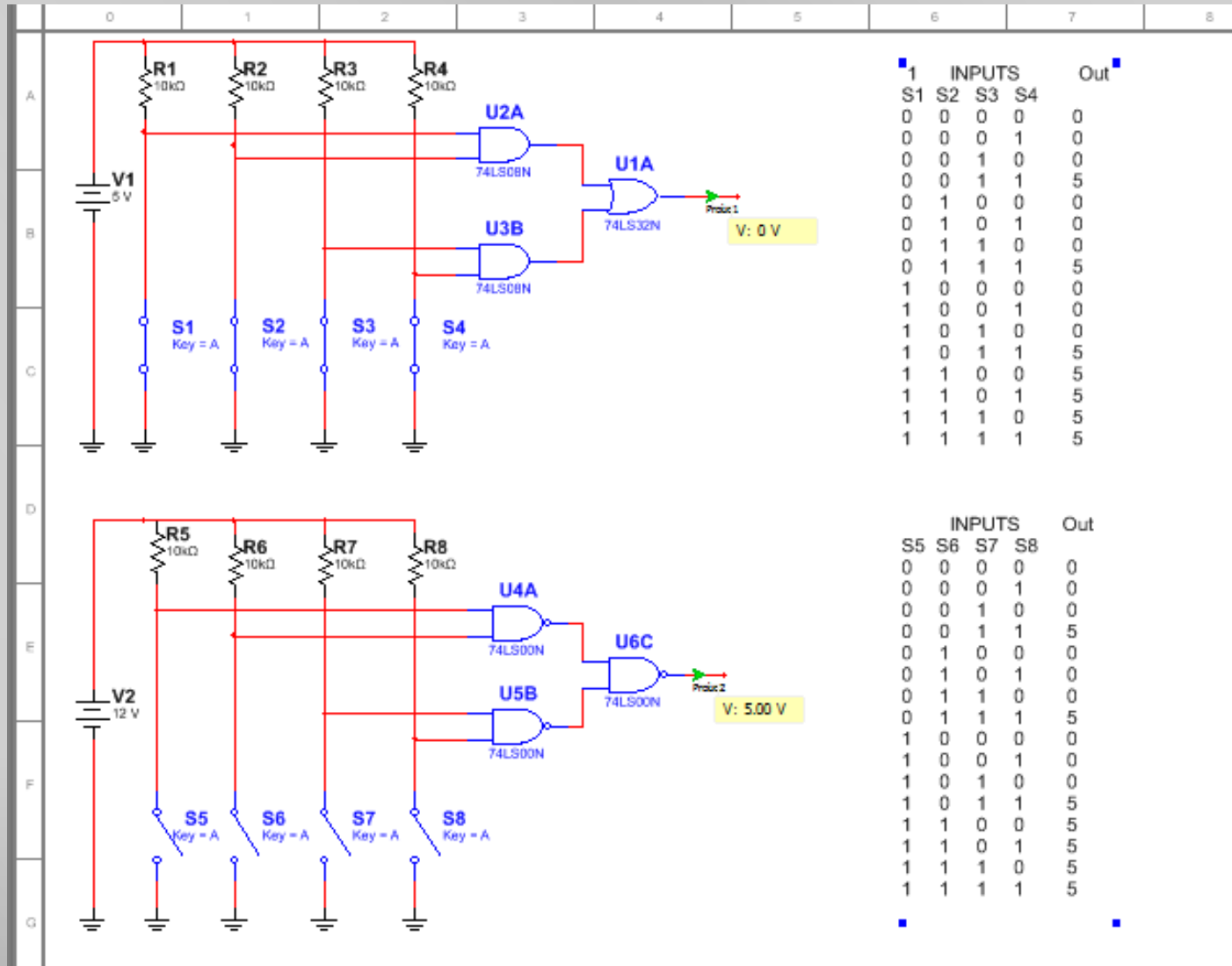


Simplify Circuit Example #1

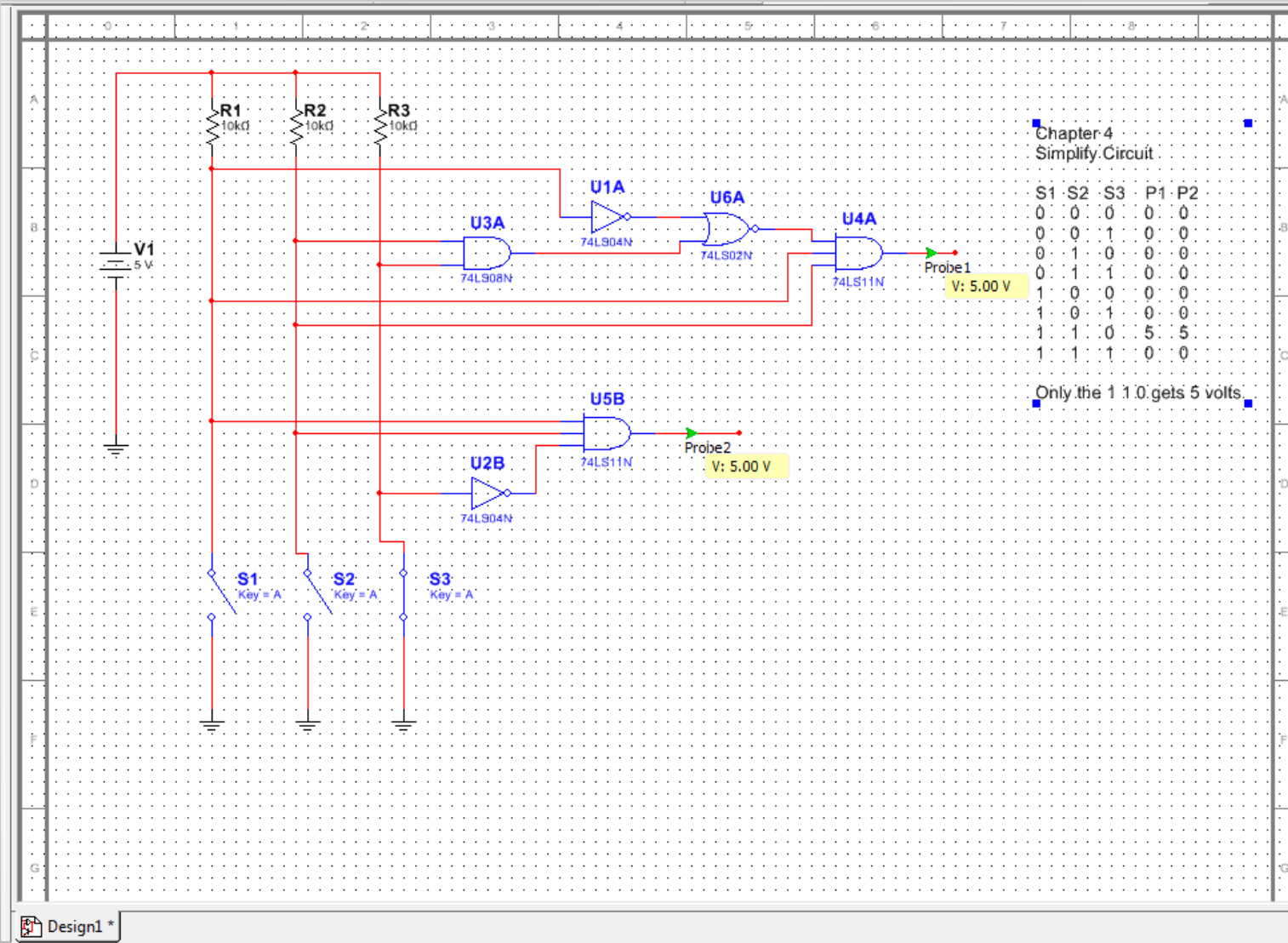

Simplify Circuit Example #2

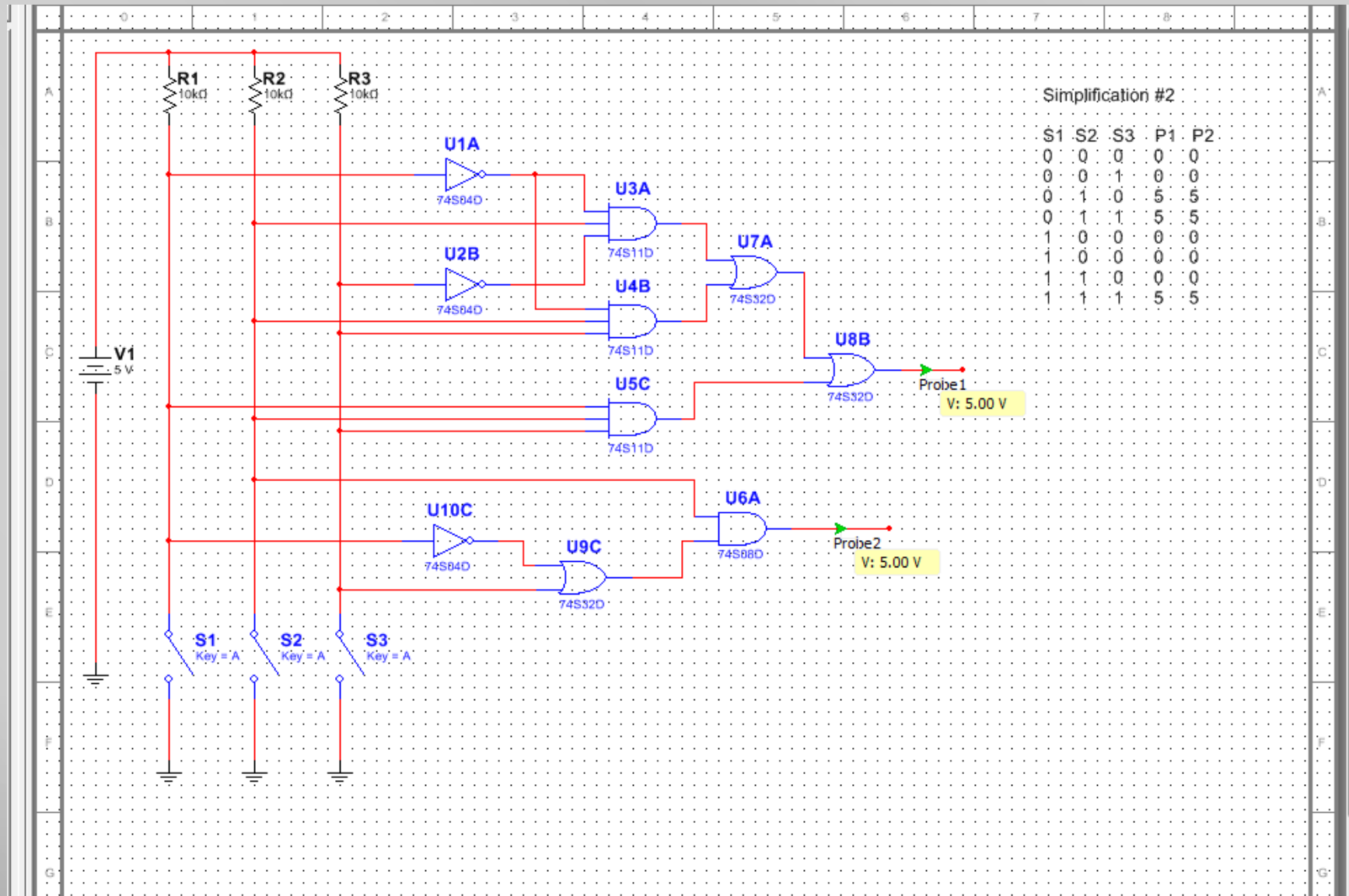

Exclusive NOR

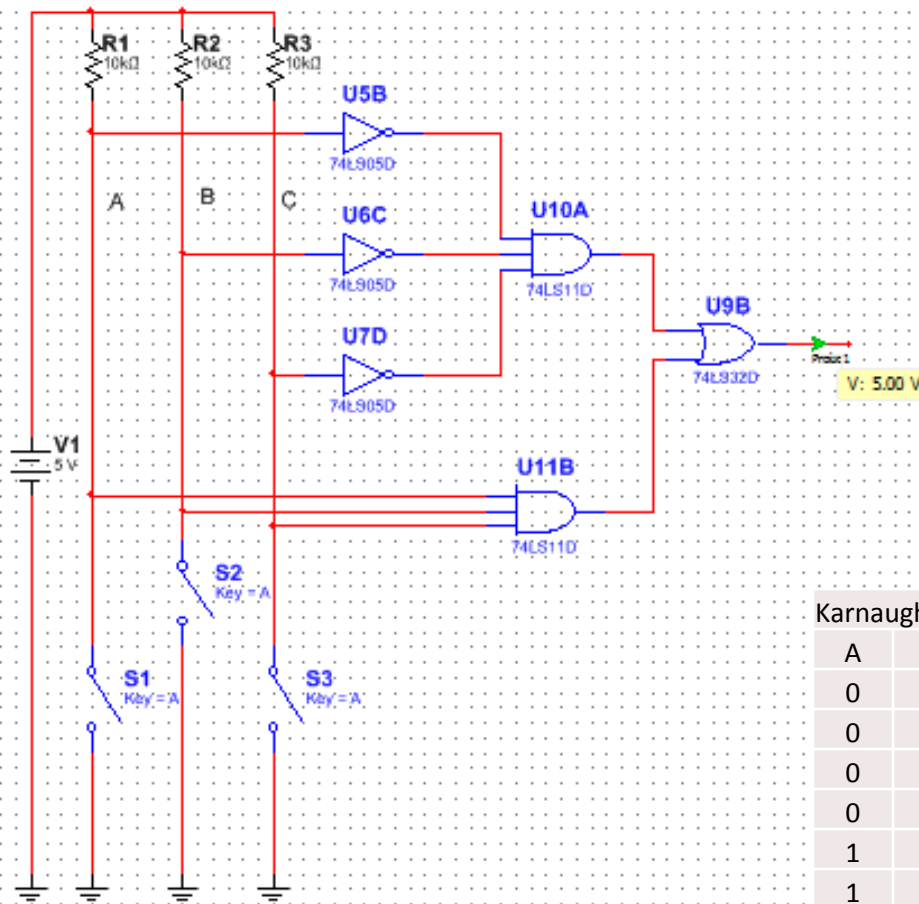


Exclusive NOR

A	B	C	Out
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


Karnaugh Mapping

A	B	C	X		C'	C
0	0	0	1	A'B'	1	0
0	0	1	0	A'B	0	0
0	1	0	0	AB	0	1
0	1	1	0	AB'	0	0
1	0	0	0			
1	0	1	0			
1	1	0	0			
1	1	1	1			


Exclusive OR

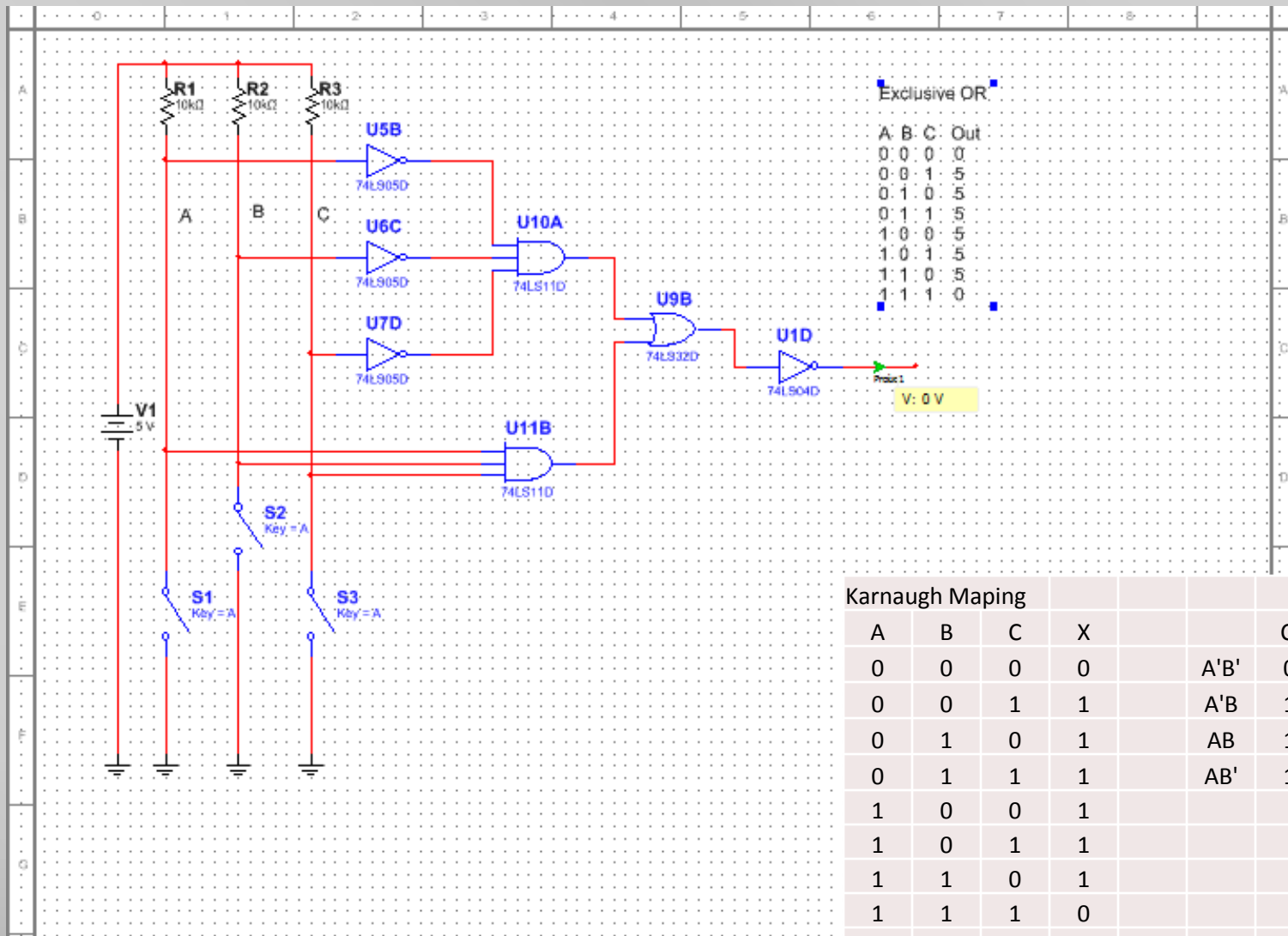


Gates with XOR & XNOR

 


LABS

 

ELVIS Lab with Multisim Verification

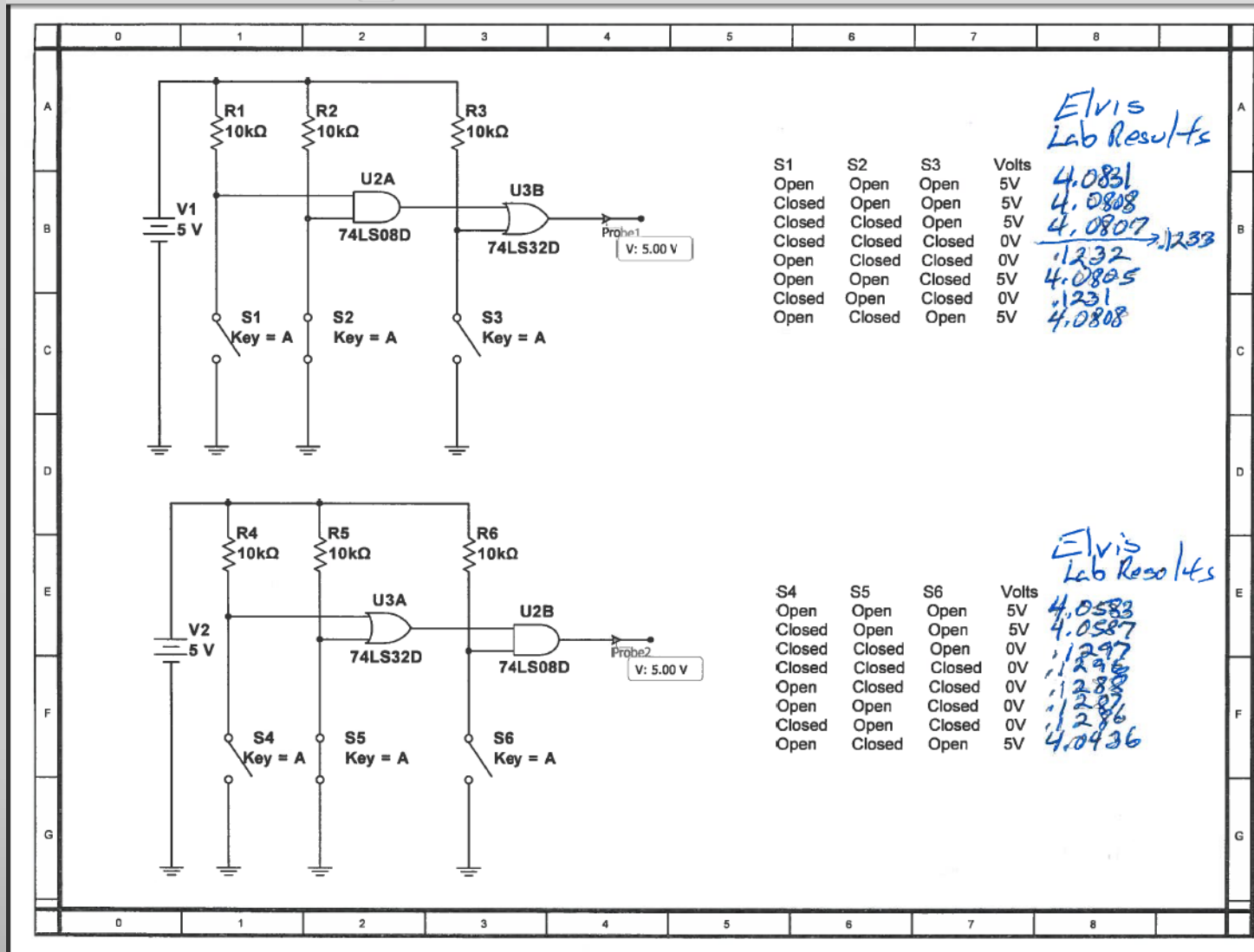

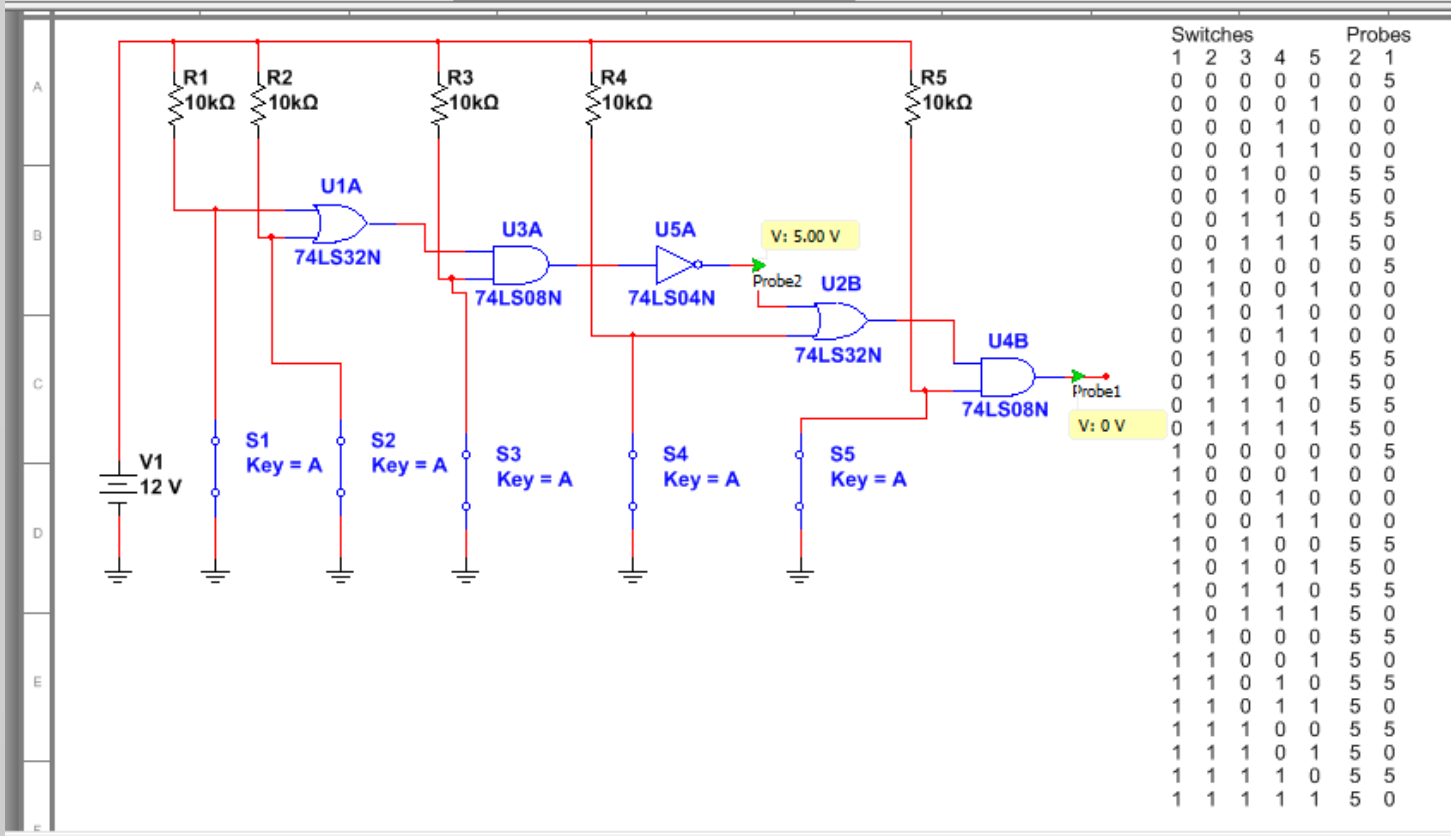Lecture 3, Simulated on MultiSim and in LAB




Switches					Probes	
1	2	3	4	5	2	1
1	0	0	0	0	0	5
0	0	0	0	0	1	0
0	0	0	0	1	0	0
0	0	0	1	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	5	5
0	0	1	0	1	5	0
0	0	1	1	0	5	5
0	0	1	1	1	5	0
0	1	0	0	0	0	5
0	1	0	0	1	0	0
0	1	0	1	0	0	0
0	1	0	1	1	0	0
0	1	1	0	0	5	5
0	1	1	0	1	5	0
0	1	1	1	0	0	0
1	0	0	0	0	0	5
1	0	0	0	1	0	0
1	0	0	1	0	0	0
1	0	0	1	1	0	0
1	0	1	0	0	5	5
1	0	1	0	1	5	0
1	0	1	1	0	5	5
1	0	1	1	1	5	0
1	1	0	0	0	5	5
1	1	0	0	1	5	0
1	1	0	1	0	5	5
1	1	0	1	1	5	0
1	1	1	0	0	5	5
1	1	1	0	1	5	0
1	1	1	1	0	5	5
1	1	1	1	1	5	0

LAB Lecture 3						
5 Gate Input Results						
S1	S2	S3	S4	S5	Probe	
0	0	0	0	0	0	5.156
0	0	0	0	1	0	0.1342
0	0	0	1	0	0	0.1362
0	0	0	1	1	0	0.1343
0	0	1	0	0	0	5.161
0	0	1	0	1	0	0.1336
0	0	1	1	0	0	5.111
0	0	1	1	1	0	0.1337
0	1	0	0	0	0	5.174
0	1	0	0	1	0	0.1337
0	1	0	1	0	0	0.1339
0	1	0	1	1	0	0.1339
0	1	1	0	0	0	5.177
0	1	1	0	1	0	0.1335
0	1	1	1	0	0	5.178
0	1	1	1	1	0	0.1334
1	0	0	0	0	0	5.176
1	0	0	0	1	0	0.1336
1	0	0	1	0	0	0.1336
1	0	0	1	1	0	0.1338
1	0	1	0	0	0	5.178
1	0	1	0	1	0	0.1334
1	0	1	1	0	0	5.178
1	0	1	1	1	0	0.1334
1	1	0	0	0	0	5.174
1	1	0	0	1	0	0.1334
1	1	0	1	0	0	5.174
1	1	0	1	1	0	0.1335
1	1	1	0	0	0	5.188
1	1	1	0	1	0	0.1333
1	1	1	1	0	0	5.182
1	1	1	1	1	0	0.1334

jn1 *

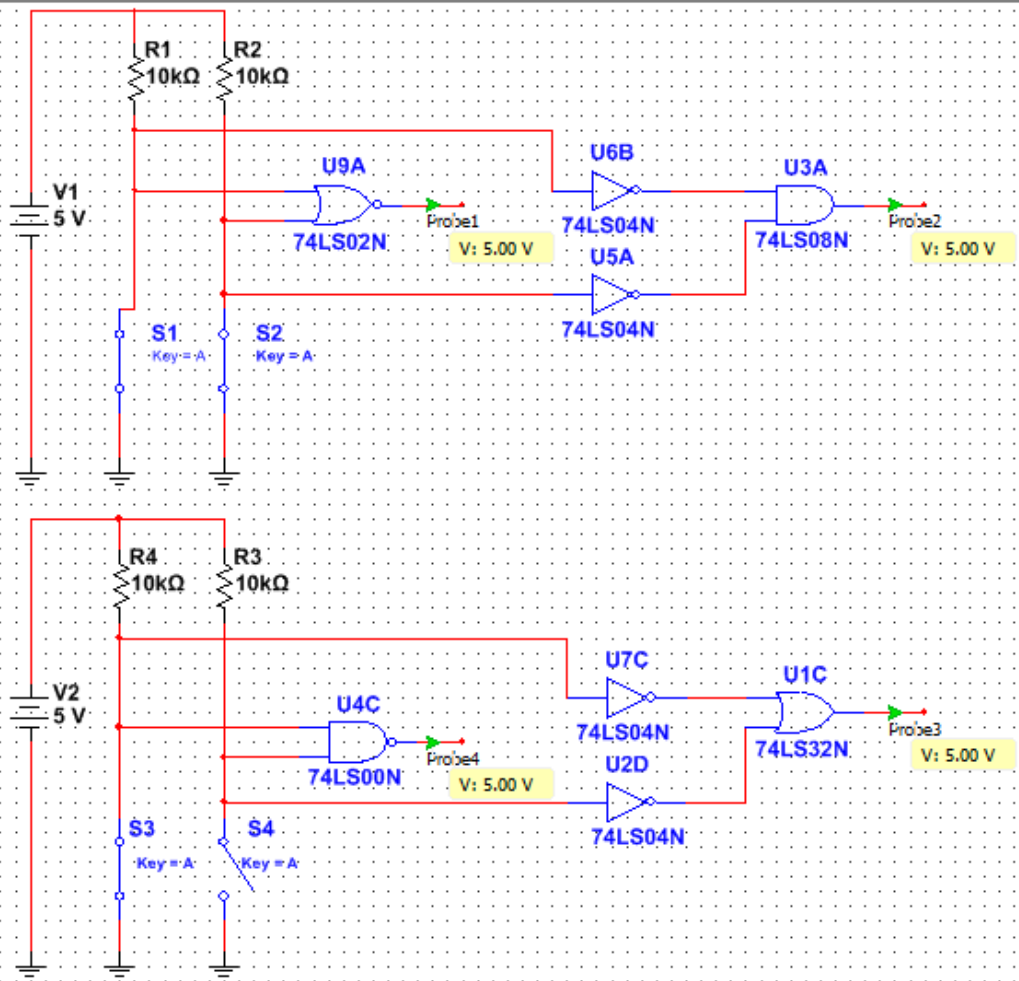DeMorgan's Theorem, Simulated on MultiSim & Lab Results



DeMorgan's Theorem #16

Input1	Input 2	Probe1	Probe 2
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Demorgan's Theorem #16

Lab Results

S1	S2	Probe 1	Probe 2
0	0	4.098	4.04
0	1	0.0861	0.1262
1	0	0.0861	0.1262
1	1	0.0861	0.1262

DeMorgan's Theorem #17

Input1	Input 2	Probe 3	Probe 4
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

Demorgan's Theorem #17

Lab Results


S1	S2	Probe 1	Probe 2
0	0	4.096	4.085
0	1	4.096	4.083
1	0	4.094	4.083
1	1	0.086	0.1262

Wrong way to do a Flip Flop


The image displays a breadboard-style circuit diagram on a grid. A 250 Hz square wave pulse generator is connected to the inputs of two 74LS90D NAND gates, labeled U1A and U2B. The outputs of these gates are connected to the Set (S) and Reset (R) inputs of an XLA1 flip-flop. The flip-flop's Clock (C) input is connected to a common ground. The flip-flop's outputs are labeled Q and T. Below the circuit, a power supply section includes a 5V source (V1), two 10kΩ resistors (R1 and R2), and a switch (S2) labeled 'Key=A'. A logic analyzer window titled 'Logic Analyzer-XLA1' is overlaid on the right side of the circuit. The window shows a timing diagram with a time scale from 0.000 to 8.000ms. The signal list on the left includes '3', '4', 'Term 3' through 'Term 16', 'Clock_Int', 'Clock_Qua', and 'Trigg_Qua'. The bottom control panel of the logic analyzer shows 'Stop', 'Reset', and 'Reverse' buttons, along with a table of trigger points (T1, T2, T2-T1) and a 'Clock' section with 'Clocks/Div' set to 8. A 'Trigger' section includes 'Set...', 'External (C) Qualifier (Q)', and 'Qualifier (T)' options.

Gate Logic Example | Flip Flop * | Design1D_sls_June 2013 *




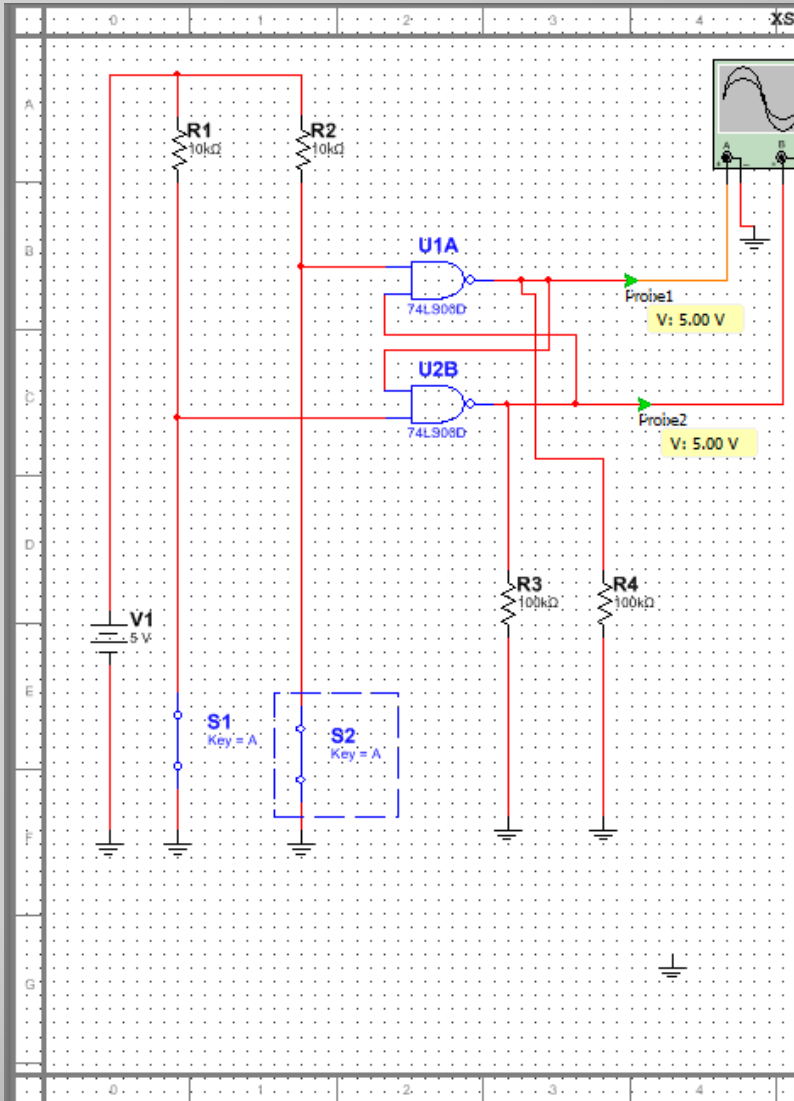
Correct Way to do a Flip Flop & Lab Results



Flip Flop Circuit			
Lab Results			
S1	S2	Q	Q/Bar
0	0	4.04	4.039
0	1	0.011	4.04
1	0	4.042	0.117
		.1262/	
1	1	4.042	0.129

 

Presentation 5: Slide 47 Lab Results

 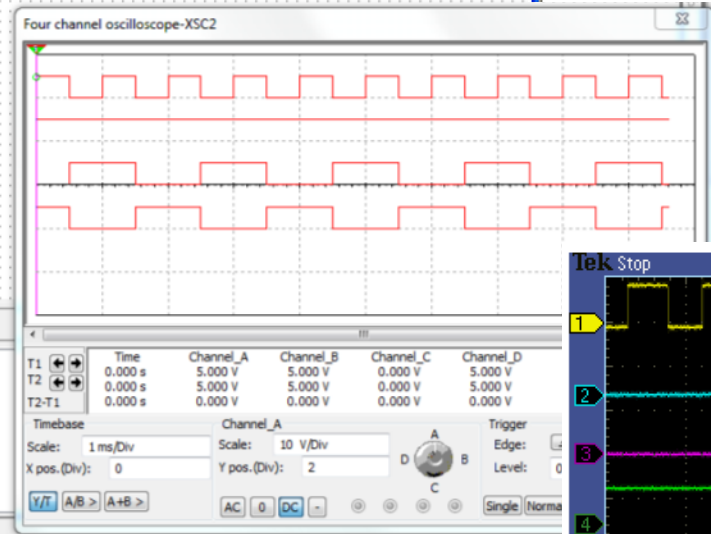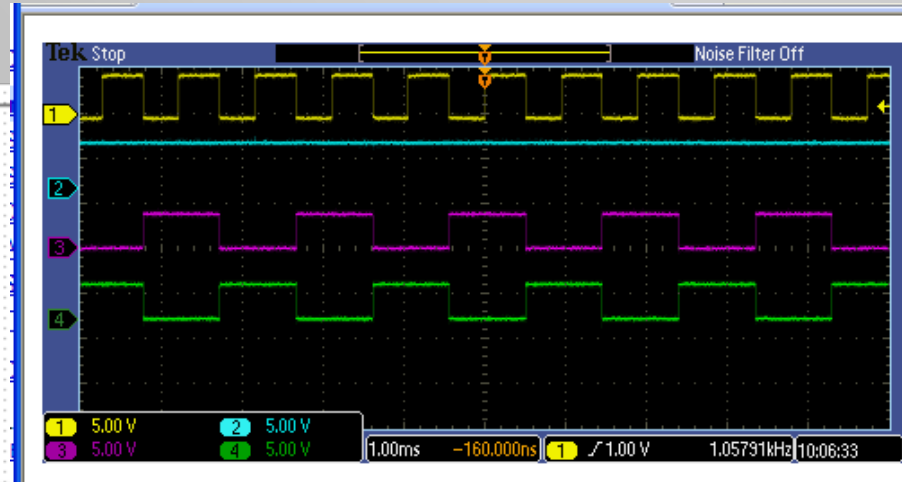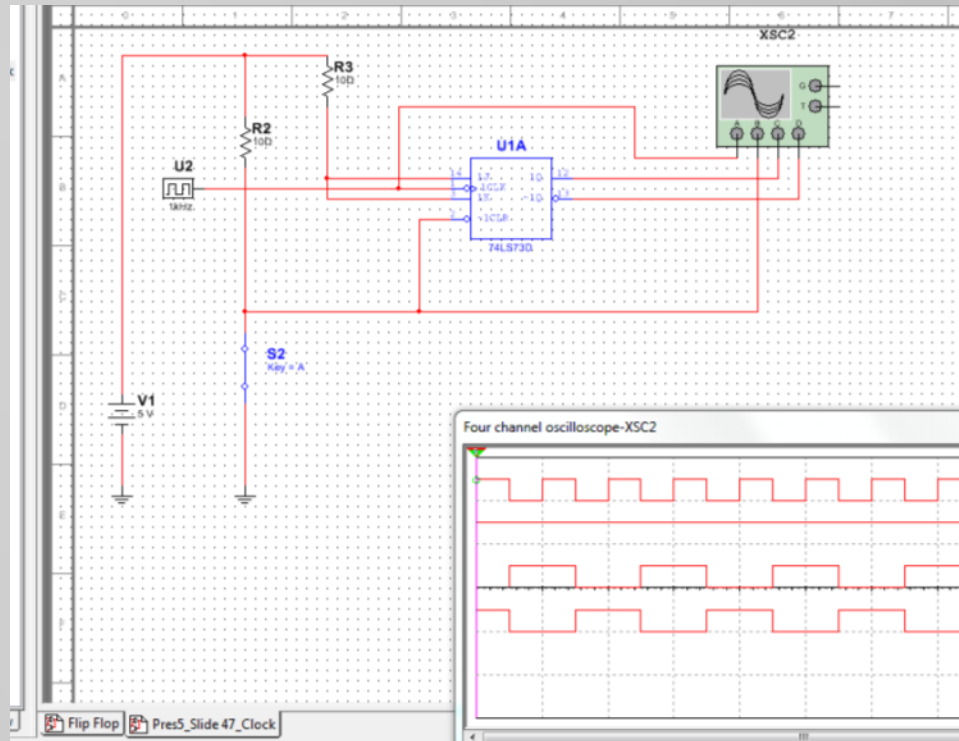

ly 22, 2013, 6:14:26 PM

Copper layers Simulation

Test Results for DeMorgan from Elvis Simulation:

DeMorgan's Theorem #16						
Probe After NOR Gate				Probe After AND Gate		
Input 1	Input 2	Volts		Input 1	Input 2	Volts
0	0	4.018		0	0	4.04
0	1	0.0861		0	1	0.1262
1	0	0.0861		1	0	0.1262
1	1	0.0861		1	1	0.1263


DeMorgan's Theorem #17						
Probe After NAND Gate				Probe After OR Gate		
Input 1	Input 2	Volts		Input 1	Input 2	Volts
0	0	4.096		0	0	4.085
0	1	4.096		0	1	4.083
1	0	4.094		1	0	4.083
1	1	0.086		1	1	0.1262

LAB: Blinking LED on Basic Stamp 2; Programming

```
'{$STAMP BS2}
'PBASIC 2.0}
'{$PORT {$COM1}
'Program 1.1/;  Blinking LED Example
Cnt      VAR      Byte      'Variable for counting
PB1      VAR      IN1       'Variable for PB1 input
LED1     CON      4         'Variable for LED1  output
INPUT 1
OUTPUT 4
LOW LED1
Start:
  IF PB1 = 0 THEN Start      'Not Pressed? Go back to loop
  GOSUB Blink_LED1          'If it was pressed then perform subroutine
GOTO Start                  'Afer return, go back to start
Blink_LED1:
  FOR Cnt = 1 TO 5          'Setup loop for 5 counts
    HIGH LED1               'Turn on LED
    PAUSE 1000              'Wait 1 second
    LOW LED1                'Turn off LED
    PAUSE 1000              'wait 1 second
  NEXT                      'Repeat loop until done
RETURN                      'return back to after gosub call
```

See Next Slide . . .

 Blinking LED LAB using Basic Stamp 2 & BoE



Components:

1. LED Yellow
2. 220 ohm resistor
3. Push button
4. 10 k-ohm resistor
5. Board of Education

To watch a video of our blinking LED go to:

<http://www.youtube.com/watch?v=zJ55SocmE8Y>

Basic Stamp 2, Temperature Control check using a potentiometer. Program ->

See Next Slide

```
Basic Stamp 2, Temp change with potentiometer
'{$STAMP BS2}
'Program 1.2, Simple Heater
LED1    VAR    OUT4
RC      CON    7
Temp    VAR    Word

OUTPUT 4
LED1 = 1

Main:
  GOSUB ReadTemp
  GOSUB Checktemp
  PAUSE 250
GOTO Main

ReadTemp
HIGH RC
PAUSE 10
RCTIME RC, 1, Temp
Temp = Temp/30

  DEBUG "Temp = ", dec Temp, CR
RETURN


CheckTemp:

  IF (Temp > 100) OR (LED1 = 1) THEN Checkoff
  LED1 = 1
  DEBUG "The heater energized", CR

Checkoff:
  IF (Temp < 120) OR (LED1 = 0) THEN Checkdone
  LED1 = 0
  DEBUG "The heater de-energized", CR

Checkdone:
RETURN
```



Heater Control

 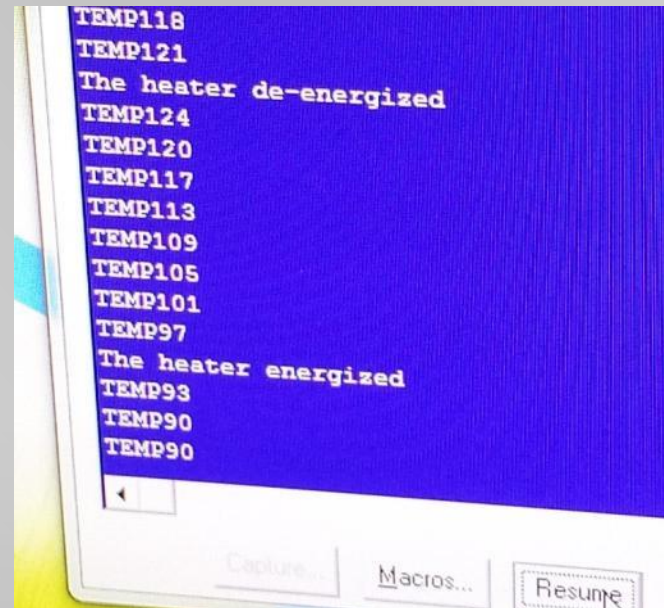


See the video of how this works at:

<http://youtu.be/hX5S-4GpeyI>

Adding a potentiometer (10K) and a capacitor (1 Uf) to the original Blinking light circuit, we were able to turn the LED on and off using the potentiometer. Of course a new program was written to control this as well. See Below:



 Heater Control Programming with Stamp Plot Lite



Screen Shot of changing the potentiometer

Heater Display with StampPlot Lite

```
'($STAMP BS2)
'Program 1.2, Simple Heater
PAUSE 500
DEBUG "!SPAN 50,150",CR
DEBUG "!TMAX 60",CR
DEBUG "!PNTS 500",CR
DEBUG "!TITL Simple Heater Control",CR
DEBUG "!SHET ON",CR
DEBUG "!TSMP ON",CR
DEBUG "!PLOT ON",CR
DEBUG "!RSET",CR
```

```
LED1 VAR OUT4
RC CON 7
Temp VAR Word
```

```
OUTPUT 4
LED1 = 1
```

```
Main:
GOSUB ReadTemp
GOSUB CheckTemp
PAUSE 250
GOTO Main
```

```
ReadTemp
HIGH RC
PAUSE 10
RCTIME RC, 1, Temp
Temp = Temp/30
```

```
DEBUG DEC Temp, CR
DEBUG IBIN LED1, CR

DEBUG "Temp = " DEC Temp, CR
RETURN
```


```
CheckTemp:

IF (Temp > 100) OR (LED1 = 1) THEN Checkoff
LED1 = 1
DEBUG "The heater energized", CR
DEBUG "!USRC The heater is energized!", CR
```

```
Checkoff:
IF (Temp < 120) OR (LED1 = 0) THEN Checkdone
LED1 = 0
DEBUG "The heater de-energized", CR
DEBUG "!USRS The heater is de-energized!", CR
```

```
Checkdone:
RETURN
```


Picture of our Binary Code LED Flasher

 



FINAL PROJECT

7 Segment LED displaying a sequential count of the hexadecimal numbers 1 thru 9 then A thru F.
This is followed by tones from a speaker playing . . .
Frere Jacques!

Final Project Program Code for 7 segment LED with Speaker Output

EECT 112 Final Project: Jeff Noggle & Steve Smith

Display the digits 0 through 9, and A thru F on a 7-segment LED display, then play the first few notes from Frere Jacques

```
{ $STAMP BS2 }
{ $PBASIC 2.5 }

DEBUG "Program Running!"


OUTH = %00000000      ' OUTH initialized to low.
DIRH = %11111111      ' Set P8-P15 to all output-low.

' Digit:
' BAFG.CDE
OUTH = %00011000      ' 0
PAUSE 1500
OUTH = %01111011      ' 1
PAUSE 1500
OUTH = %00101100      ' 2
PAUSE 1500
OUTH = %00101001      ' 3
PAUSE 1500
OUTH = %01001011      ' 4
PAUSE 1500
OUTH = %10001001      ' 5
PAUSE 1500
OUTH = %10001000      ' 6
PAUSE 1500
OUTH = %00111011      ' 7
PAUSE 1500
OUTH = %00001000      ' 8
PAUSE 1500
OUTH = %00001001      ' 9
PAUSE 1500
OUTH = %00001010      ' A
PAUSE 1500
OUTH = %11001000      ' b
PAUSE 1500
OUTH = %10011100      ' c
PAUSE 1500
OUTH = %01101000      ' d
PAUSE 1500
OUTH = %10001100      ' e
PAUSE 1500
OUTH = %10001110      ' f
PAUSE 1500

                                (Program continued)
                                DIRH = %00000000      ' I/O pins to input,
                                                                ' segments off.
                                Play the first few notes from Frere Jacques.
                                Notes DATA "C","D","E","C","C","D","E","C","E","F",
                                "G","E","F","G","Q"
                                Durations DATA 4,4,4,4,4,4,4,4,4,4,
                                2,4,4,2
                                WholeNote CON 2000
                                index VAR Byte
                                offset VAR Nib
                                noteLetter VAR Byte
                                noteFreq VAR Word
                                noteDuration VAR Word
                                DO UNTIL noteLetter = "Q"
                                READ Notes + index, noteLetter
                                LOOKDOWN noteLetter, [ "A", "b", "B", "C", "d",
                                "D", "e", "E", "F", "g",
                                "G", "a", "P", "Q" ], offset
                                LOOKUP offset, [ 1760, 1865, 1976, 2093, 2217,
                                2349, 2489, 2637, 2794, 2960,
                                3136, 3322, 0, 0 ], noteFreq
                                READ Durations + index, noteDuration
                                noteDuration = WholeNote / noteDuration
                                FREQOUT 1, noteDuration, noteFreq
                                index = index + 1

                                LOOP
                                END
```

 Picture: Board of Education Final Project



Materials:

7 – 1K resistors

1 – 7 segment LED
LN513RA

1 – 8 Ohm Speaker

Many Wires


We removed the one resistor and changed to a direct wire to get a brighter display.

Please enjoy Frere Jacques !!!!

Trials and Tribulations of the Final Project

We found that we were still having an issue with the display and it would not show the 0 thru F as we wanted to see it.

Finally we wrote down what we were seeing and noticed a pattern:

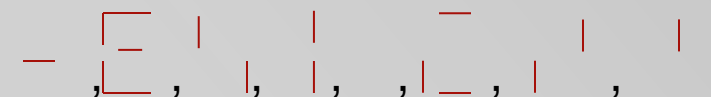 which was giving us the missing parts of the numbers.


Therefore we established we needed to reverse what our code was being sent to the controller. Once we switched the program for our data strings we got the correct numbers and letters showing on the 7 segment LED. We added the finale of Frere Jacques!

At one point, we also had a wire that was not fully inserted into the board for the 'c' segment of the LED but that was quickly rectified.


Go to next Slide for the link to the Video of our final project!

WOO HOO!!!

<http://youtu.be/-DDEgVoWwul>

 

ADDITIONAL DATA

 

Alternate Logic-Gate Representations (From Class)

- To convert a standard symbol to an alternate:
 - Invert each input and output in standard symbols.


Add an inversion bubble where there are none.

Remove bubbles where they exist.




Boolean Theorems Continued...

3-10 Boolean Theorems

 


$$(1) \quad x \cdot 0 = 0$$

 Theorem (2) is also obvious by comparison with ordinary multiplication.




$$(2) \quad x \cdot 1 = x$$

 

$$(3) \quad x \cdot x = x$$

 Theorem (4) can be proved in the same manner.



$$(4) \quad x \cdot \bar{x} = 0$$

Theorem (1) states that if any variable is ANDed with 0, the result must be 0.

Prove Theorem (3) by trying each case.

If $x = 0$, then $0 \cdot 0 = 0$


If $x = 1$, then $1 \cdot 1 = 1$

Thus, $x \cdot x = x$

Boolean Theorems

Done


3-10 Boolean Theorems

 

 
(5) $x + 0 = x$

Theorem (5) is straightforward, as 0 added to anything does not affect value, either in regular addition or in OR addition.

Theorem (6) states that if any variable is ORed with 1, the is always 1. Check values: $0 + 1 = 1$ and $1 + 1 = 1$.




(6) $x + 1 = 1$

 

(7) $x + x = x$

Theorem (7) can be proved by checking for both values of x: $0 + 0 = 0$ and $1 + 1 = 1$.

Theorem (8) can be proved similarly.

 


(8) $x + \bar{x} = 1$

FLIP-FLOP using NAND Gates

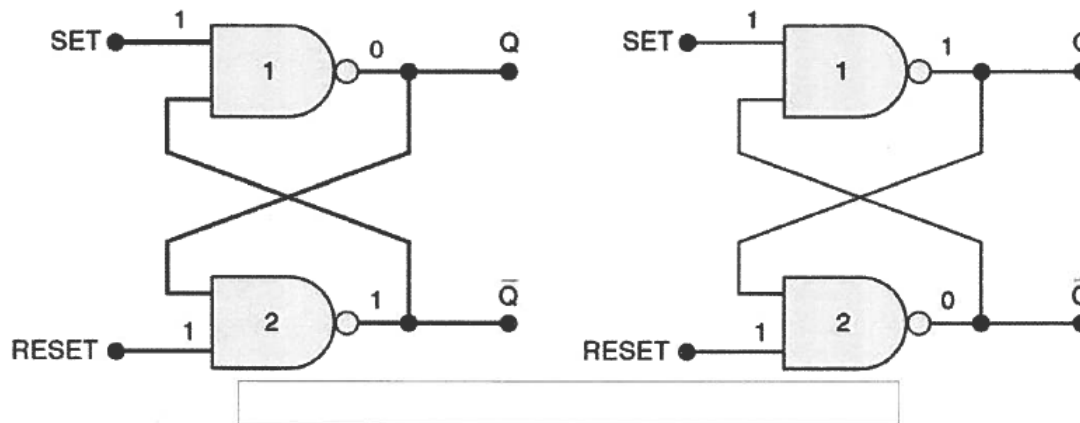5-1 NAND Gate Latch

- The **NAND** gate latch or simply latch is a basic FF.
 - Inputs are *SET* and *CLEAR (RESET)*.
- Inputs are active-LOW—output will change when the input is pulsed LOW.
 - When the latch is set: $Q = 1$ and $\bar{Q} = 0$
 - When the latch is clear or reset: $Q = 0$ and $\bar{Q} = 1$



The following pages contain Chip Diagrams

2 input NOR Gate

SDLS027

SN5402, SN54LS02, SN54S02, SN7402, SN74LS02, SN74S02 QUADRUPLE 2-INPUT POSITIVE-NOR GATES

DECEMBER 1983—REVISED MARCH 1988

- Package Options include Plastic "Small Outline" Packages, Ceramic Chip Carriers and Flat Packages, and Plastic and Ceramic DIPs
- Dependable Texas Instruments Quality and Reliability

description

These devices contain four independent 2-input-NOR gates.


The SN5402, SN54LS02, and SN54S02 are characterized for operation over the full military temperature range of -55°C to 125°C . The SN7402, SN74LS02, and SN74S02 are characterized for operation from 0°C to 70°C .

FUNCTION TABLE (each gate)


INPUTS		OUTPUT
A	B	Y
H	X	L
X	H	L
L	L	H

SN5402 . . . J PACKAGE
SN54LS02, SN54S02 . . . J OR W PACKAGE
SN7402 . . . N PACKAGE
SN74LS02, SN74S02 . . . D OR N PACKAGE

(TOP VIEW)

 

SN5402 . . . W PACKAGE
(TOP VIEW)

 

Inverter Diagram

- Dependable Texas Instruments Quality and Reliability


description/ordering information

These devices contain six independent inverters.


SN5404, SN54LS04, SN54S04, SN7404, SN74LS04, SN74S04 HEX INVERTERS

SDLS029C - DECEMBER 1983 - REVISED JANUARY 2004

SN5404 . . . J PACKAGE
SN54LS04, SN54S04 . . . J OR W PACKAGE
SN7404, SN74S04 . . . D, N, OR NS PACKAGE
SN74LS04 . . . D, DB, N, OR NS PACKAGE
(TOP VIEW)

 

SN5404 . . . W PACKAGE
(TOP VIEW)

 

SN54LS04, SN54S04 . . . FK PACKAGE
(TOP VIEW)

AND Gate

SN5408, SN54LS08, SN54S08 SN7408, SN74LS08, SN74S08 QUADRUPLE 2-INPUT POSITIVE-AND GATES

SDLS033 – DECEMBER 1983 – REVISED MARCH 1988

- Package Options Include Plastic “Small Outline” Packages, Ceramic Chip Carriers and Flat Packages, and Plastic and Ceramic DIPs
- Dependable Texas Instruments Quality and Reliability

description

These devices contain four independent 2-input AND gates.

The SN5408, SN54LS08, and SN54S08 are characterized for operation over the full military temperature range of -55°C to 125°C . The SN7408, SN74LS08 and SN74S08 are characterized for operation from 0° to 70°C .


FUNCTION TABLE (each gate)

INPUTS		OUTPUT
A	B	Y
H	H	H
L	X	L
X	L	L

Logic symbol†


SN5408, SN54LS08, SN54S08 . . . J OR W PACKAGE
SN7408 . . . J OR N PACKAGE
SN74LS08, SN74S08 . . . D, J OR N PACKAGE

(TOP VIEW)

 

SN54LS08, SN54S08 . . . FK PACKAGE

(TOP VIEW)

 

OR Gate

SDLS100

SN5432, SN54LS32, SN54S32, SN7432, SN74LS32, SN74S32 QUADRUPL 2-INPUT POSITIVE-OR GATES

DECEMBER 1983 - REVISED MARCH 1989

- Package Options Include Plastic "Small Outline" Packages, Ceramic Chip Carriers and Flat Packages, and Plastic and Ceramic DIPs
- Dependable Texas Instruments Quality and Reliability

description


These devices contain four independent 2-input OR gates.

The SN5432, SN54LS32 and SN54S32 are characterized for operation over the full military range of -55°C to 125°C . The SN7432, SN74LS32 and SN74S32 are characterized for operation from 0°C to 70°C .


FUNCTION TABLE (each gate)

INPUTS		OUTPUT
A	B	Y
H	X	H
X	H	H
L	L	L

 SN5432, SN54LS32, SN54S32 . . . J OR W PACKAGE
SN7432 . . . N PACKAGE
SN74LS32, SN74S32 . . . D OR N PACKAGE
(TOP VIEW)



SN54LS32, SN54S32 . . . FK PACKAGE
(TOP VIEW)

 

Triple 3-Input AND Gate

SN54LS11, SN54S11, SN74LS11, SN74S11 TRIPLE 3-INPUT POSITIVE-AND GATES

SDLS131 - APRIL 1985 - REVISED MARCH 1988

- Package Options Include Plastic "Small Outline" Packages, Ceramic Chip Carriers and Flat Packages, and Plastic and Ceramic DIPs
- Dependable Texas Instruments Quality and Reliability

description

These devices contain three independent 3-input AND gates.

The SN54LS11 and SN54S11 are characterized for operation over the full military temperature range of -55°C to 125°C . The SN74LS11 and SN74S11 are characterized for operation from 0°C to 70°C .

FUNCTION TABLE (each gate)


INPUTS			OUTPUT
A	B	C	Y
H	H	H	H
L	X	X	L
X	L	X	L
X	X	L	L

logic symbol†




SN54LS11, SN74S11 . . . J OR W PACKAGE
SN74LS11, SN74S11 . . . D OR N PACKAGE

(TOP VIEW)

 

SN54LS11, SN54S11 . . . FK PACKAGE

(TOP VIEW)

 

NC—No internal connection

logic diagram (positive logic)



Dual J-K Flip-Flops w/Clear

SN5473, SN54LS73A, SN7473, SN74LS73A DUAL J-K FLIP-FLOPS WITH CLEAR

SDLS118 – DECEMBER 1983 – REVISED MARCH 1988

- Package Options Include Plastic "Small Outline" Packages, Flat Packages, and Plastic and Ceramic DIPs
- Dependable Texas Instruments Quality and Reliability


description

The '73, and 'H73, contain two independent J-K flip-flops with individual J-K, clock, and direct clear inputs. The '73, and 'H73, are positive pulse-triggered flip-flops. J-K input is loaded into the master while the clock is high and transferred to the slave on the high-to-low transition. For these devices the J and K inputs must be stable while the clock is high.

The 'LS73A contains two independent negative-edge-triggered flip-flops. The J and K inputs must be stable one setup time prior to the high-to-low clock transition for predictable operation. When the clear is low, it overrides the clock and data inputs forcing the Q output low and the \bar{Q} output high.

The SN5473, SN54H73, and the SN54LS73A are characterized for operation over the full military temperature range of -55°C to 125°C . The SN7473, and the SN74LS73A are characterized for operation from 0°C to 70°C .

 SN5473, SN54LS73A . . . J OR W PACKAGE
SN7473 . . . N PACKAGE
SN74LS73A . . . D OR N PACKAGE
(TOP VIEW)



73
FUNCTION TABLE

INPUTS				OUTPUTS	
CLR	CLK	J	K	Q	\bar{Q}
L	X	X	X	L	H
H	\downarrow	L	L	Q_0	\bar{Q}_0
H	\downarrow	H	L	H	L
H	\downarrow	L	H	L	H
H	\downarrow	H	H	TOGGLE	

'LS73A
FUNCTION TABLE

INPUTS				OUTPUTS	
CLR	CLK	J	K	Q	\bar{Q}
L	X	X	X	L	H
H	\downarrow	L	L	Q_0	\bar{Q}_0
H	\downarrow	H	L	H	L
H	\downarrow	L	H	L	H