

Roeback's Final Project_EECT111

1


Using MultiSim, Excel and hand calculations create a set of notes that show how to:

- 1.) Combine multiple resistors in series and parallel.
- 2.) By example calculate R_T , I_T , P_T , and all the nodal voltages, branch currents and power dissipation of a resistor network.
- 3.) By example calculate the Thevenin Resistance and Voltage of a resistor network.
- 4.) Multiple capacitors combine in series and parallel.
- 5.) Using a simple RC circuit determine the
 - a.) Time Constant
 - b.) Create a graph that shows the RC time constant as a function of time
 - c.) Determine X_C at a fixed frequency
 - d.) Create a graph that shows how X_C changes as a function of frequency
- 6.) Multiple inductors combine in series and parallel.
- 7.) Using a simple RL circuit determine the
 - a.) Time Constant
 - b.) Create a graph that shows the RL time constant as a function of time
 - c.) Determine X_L at a fixed frequency
 - d.) Create a graph that shows how X_L changes as a function of frequency

Combining Resistors in Series

2

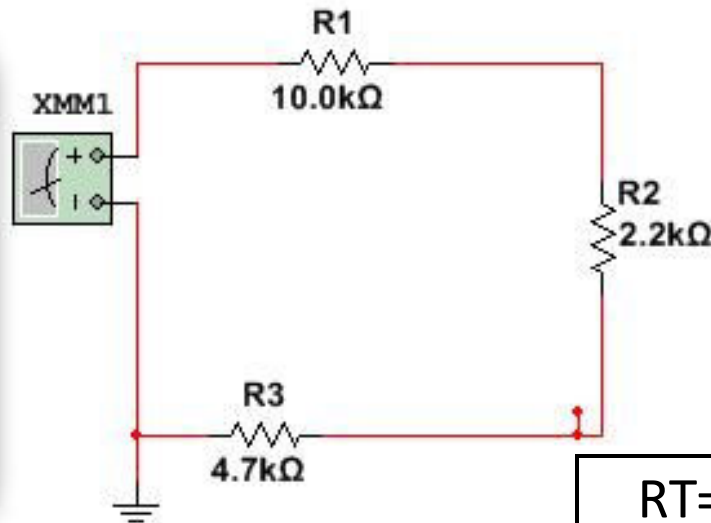The sum of all resistor values in a series circuit equals total resistance.



$R_T =$	$R_1 + R_2 + R_3 + \dots$	
$R_1 =$	$10.0E+3$	Ω
$R_2 =$	$2.2E+3$	Ω
$R_3 =$	$4.7E+3$	Ω
$R_T =$	$16.9E+3$	Ω

Combining Resistors in Parallel

3


3 approaches can be taken to calculate total resistance in parallel.

- For two or more resistors of equal value $[R1/Rn]$
(Any Resistor value / # of Resistors) can be used.
- For two resistors of any value $[(R1+R2)/(R1*R2)]$
(Product of both resistor values / sum of both resistor values).
- For 3 or more resistors of any value use the reciprocal of the sum of the reciprocal of all resistor values.
 $[1/(1/R1)+(1/R2)+(1/R3)...]$

Any Resistor Value over the Number of Resistors

4

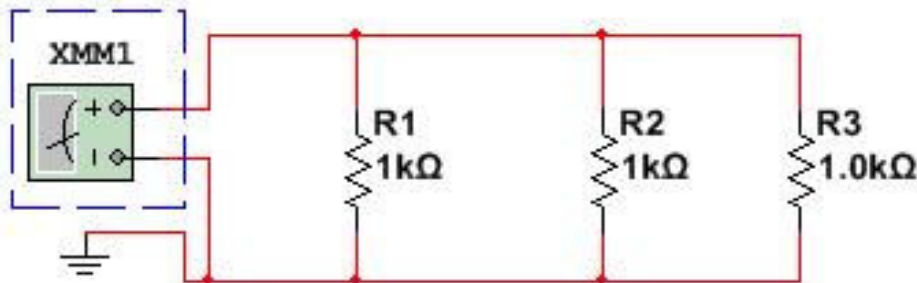This Method only works with equal value resistors in a parallel circuit.






RT=	R1/Rn	
R1=	1.0E+3	Ω
R2=	1.0E+3	Ω
R3=	1.0E+3	Ω
RT=	333.333E+0	Ω

Product over Sum Method

5

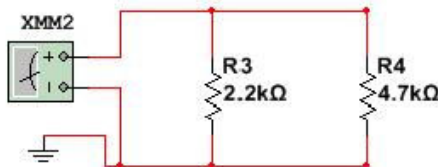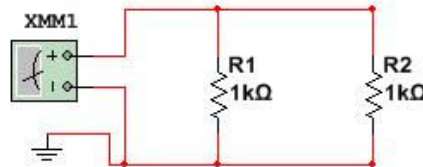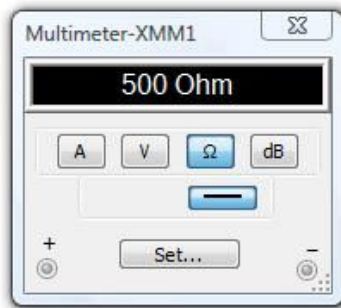This method works for two resistors of equal or different values.





RT=	$(R1 * R2) / (R1 + R2)$	
R1=	1.0E+3	Ω
R2=	1.0E+3	Ω
RT=	500.0E+0	Ω
RT=	$(R1 * R2) / (R1 + R2)$	
R3=	2.2E+3	Ω
R4=	4.7E+3	Ω
RT=	1.499E+3	Ω

The Reciprocal of the Sum of the Reciprocal Resistor Values

6

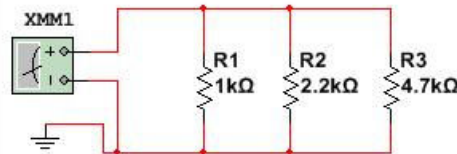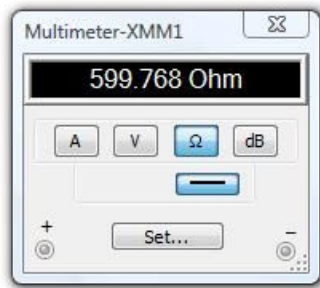This method works for calculation all parallel resistor circuits



RT=	$1/[(1/R1)+(1/R2)+(1/R3)+....]$	
R1=	1.0E+3	Ω
R2=	2.2E+3	Ω
R3=	4.7E+3	Ω
RT=	599.768E+0	Ω


- In a Series circuit total circuit resistance will always be great then the value of any single resistor within that same circuit.
- Regardless of a resistor's value within a parallel circuit, the total circuit resistance is always less.
- In a Series-Parallel circuit, the resistance of the individual parallel sub-circuits must be figured out first before figuring total circuit resistance.

The Usage of Watt & Ohm's Law

7



Calculating R_T , I_T , P_T , and all the nodal voltages, branch currents and power dissipation of a resistor network.

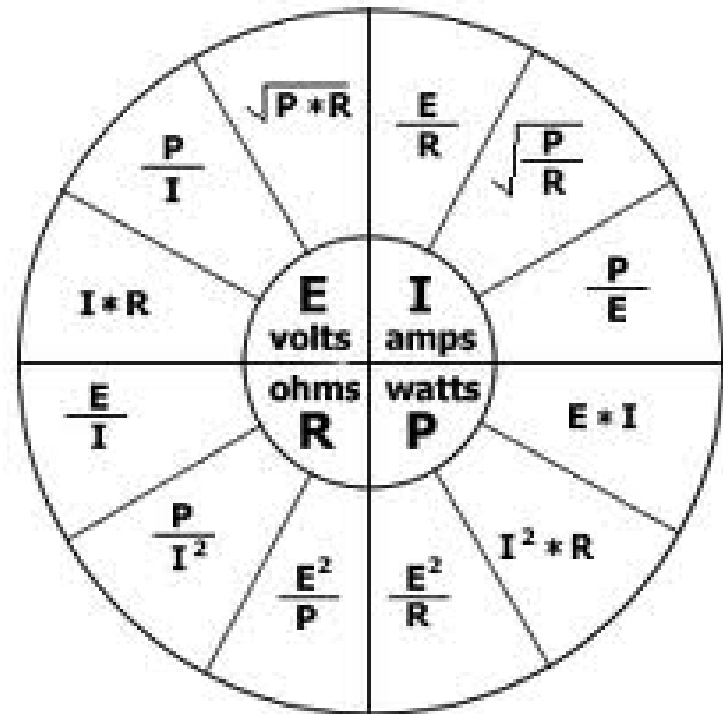- If V =Volts, R =Resistance in Ohms & I =Current in Amperes
- Ohm's Law states: $V=I \cdot R$ then:
 - $V/R=I$ and $V/I=R$
- The Watt (Power or P) = $V \cdot I$ so:
 - $P=V^2/R$ or $P=R \cdot I^2$
- With the use of these formulas the chart to the right can be made.





Ohm's Law in Series-Parallel Circuits

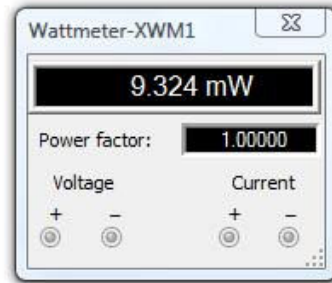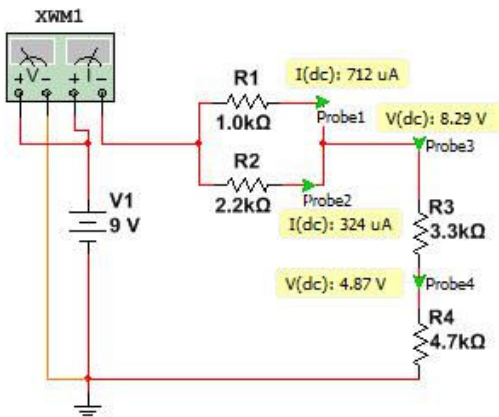The simulation proves that using the formulas (in the chart on the previous slide) we can calculate each resistors behavior within the circuit and sub-circuits.




	V1=	9 V	Amps Across	Voltage Drop	Power Consumed (W)
R1=	1.0E+3 Ω	712E-6	See Parallel	507.27E-6	
R2=	2.2E+3 Ω	324E-6	Circuit	230.58E-6	
R3=	3.3E+3 Ω	1.036E-3	3.4E+0	3.54E-3	
R4=	4.7E+3 Ω	1.036E-3	4.9E+0	5.04E-3	
R12=	687.5E+0 Ω	1.036E-3	712.2E-3	737.85E-6	
R34=	8.0E+3 Ω	1.036E-3	8.3E+0	8.59E-3	
RT=	8.688E+3 Ω	1.036E-3	9.0E+0	9.324E-3	
IT=	1.036E-3 A	SUM(R1-R4) & R12+R34		TRUE	
PT=	9.324E-3 W	Power=PT			

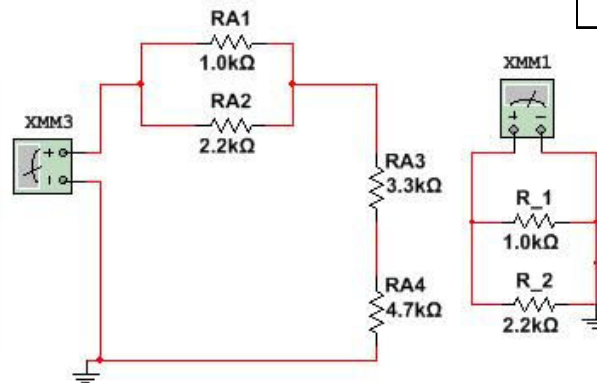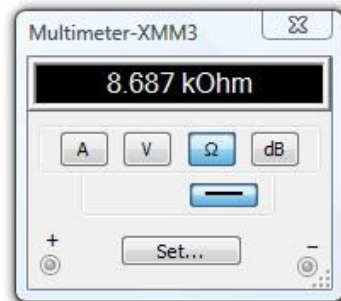

Thevenin Resistance and Voltage of a resistor network.

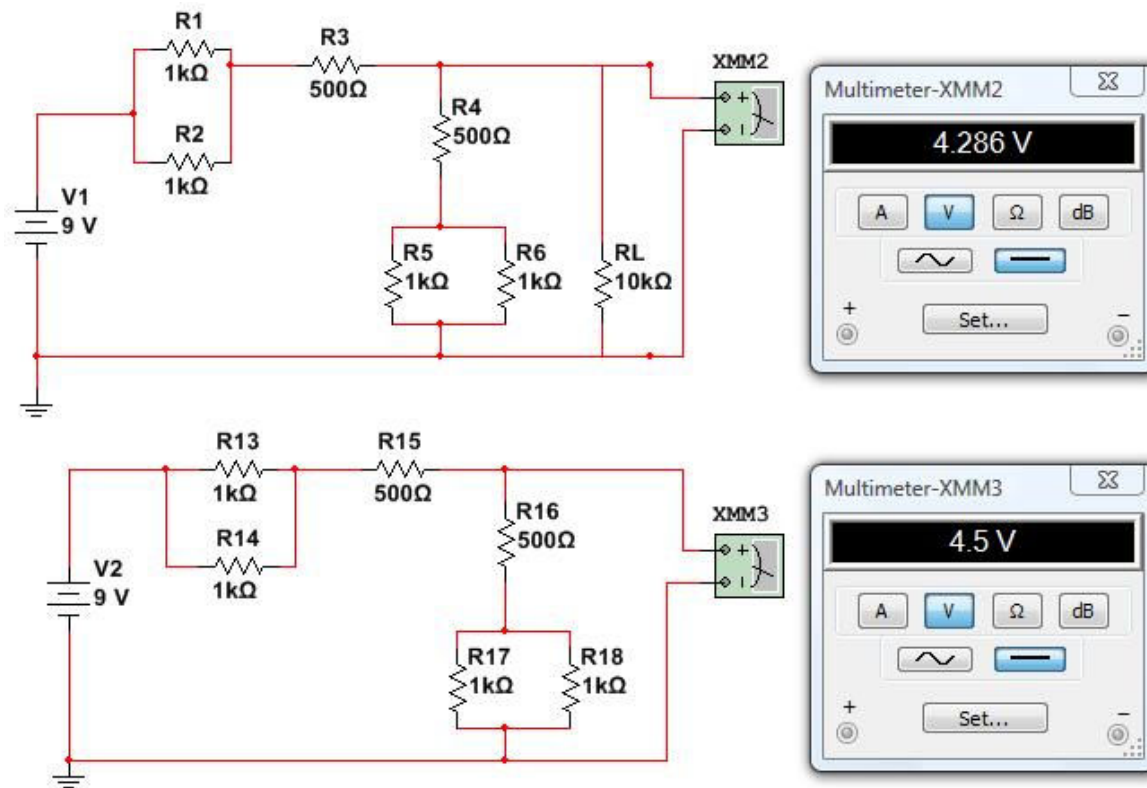To predict Thevenin Resistance and Voltage first Calculate or Measure; voltage across the existing circuit at the point of the load with the load applied then again with the load removed.





R1=	1E+3	Ω
R2=	1E+3	Ω
R3=	500E+0	Ω
R4=	500E+0	Ω
R5=	1E+3	Ω
R6=	1E+3	Ω
R12=	500E+0	Ω
R123=	1E+3	Ω
R56=	500E+0	Ω
R123456=	500E+0	Ω
R456	1E+3	Ω
RL=	10E+3	Ω
R456L=	909.091E+0	Ω
RT=	1.909E+3	Ω
V1=	9	V
Va=	4.286E+0	V
RTH=	500.0E+0	Ω
VTH=	4.5	V
VaTH=	4.286E+0	Ω
B19=B16	True	

Applying Thevenin Theorem

10

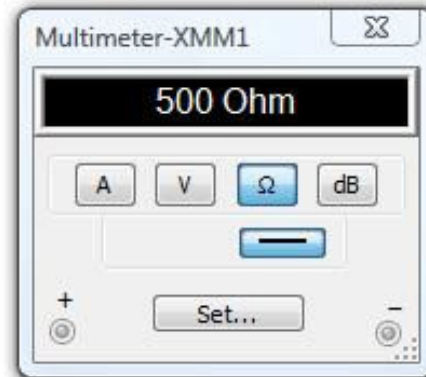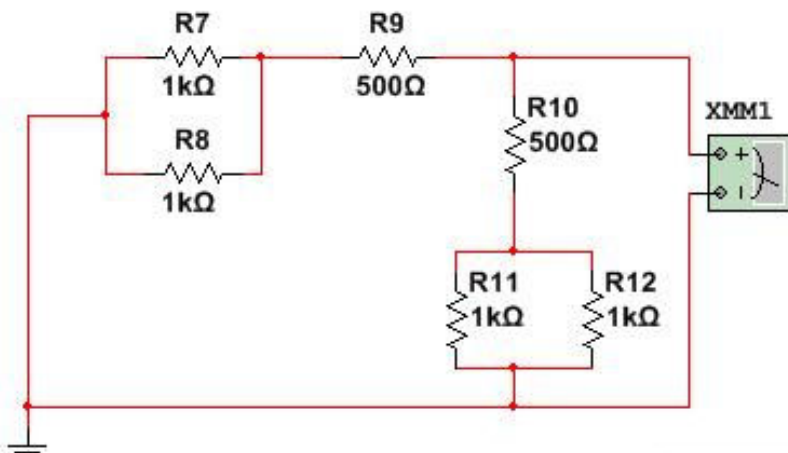Then remove the supply power and load. Short across the points the supply power was previously located and Measure or Calculate the circuit resistance at the point were the load once resided.





R1=	1E+3	Ω
R2=	1E+3	Ω
R3=	500E+0	Ω
R4=	500E+0	Ω
R5=	1E+3	Ω
R6=	1E+3	Ω
R12=	500E+0	Ω
R123=	1E+3	Ω
R56=	500E+0	Ω
R123456=	500E+0	Ω
R456	1E+3	Ω
RL=	10E+3	Ω
R456L=	909.091E+0	Ω
RT=	1.909E+3	Ω
V1=	9	V
Va=	4.286E+0	V
RTH=	500.0E+0	Ω
VTH=	4.5	V
VaTH=	4.286E+0	Ω
B19=B16	True	

Proving Thevenin Theorem

11

The circuit is replaced with a single resistor equal to that of Thevenin Resistance and the supply power is replaced with the Thevenin Voltage.

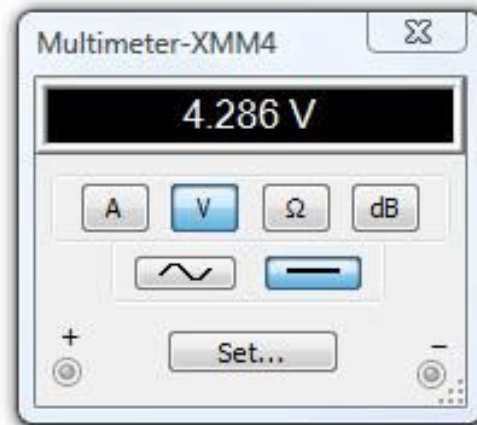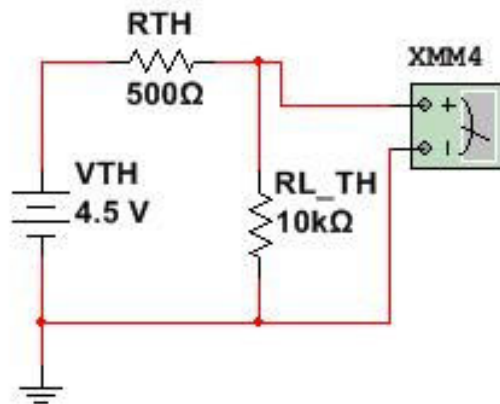The simulation supports the calculations.




R1=	1E+3	Ω
R2=	1E+3	Ω
R3=	500E+0	Ω
R4=	500E+0	Ω
R5=	1E+3	Ω
R6=	1E+3	Ω
R12=	500E+0	Ω
R123=	1E+3	Ω
R56=	500E+0	Ω
R123456=	500E+0	Ω
R456	1E+3	Ω
RL=	10E+3	Ω
R456L=	909.091E+0	Ω
RT=	1.909E+3	Ω
V1=	9	V
Va=	4.286E+0	V
RTH=	500.0E+0	Ω
VTH=	4.5	V
VaTH=	4.286E+0	Ω
B19=B16	=True	


Combining Capacitors in Parallel

12

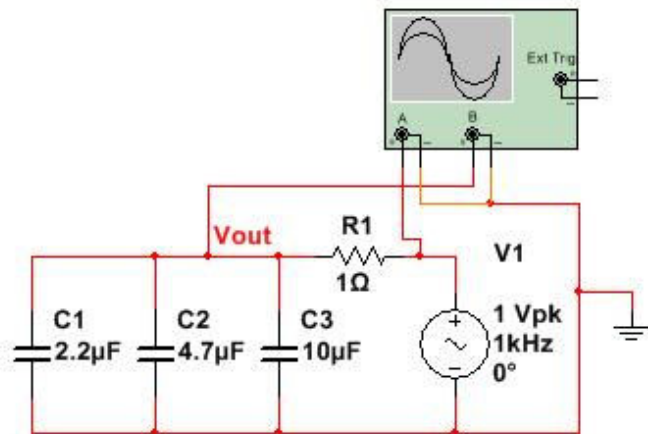The sum of all capacitor values in parallel equals total capacitance.



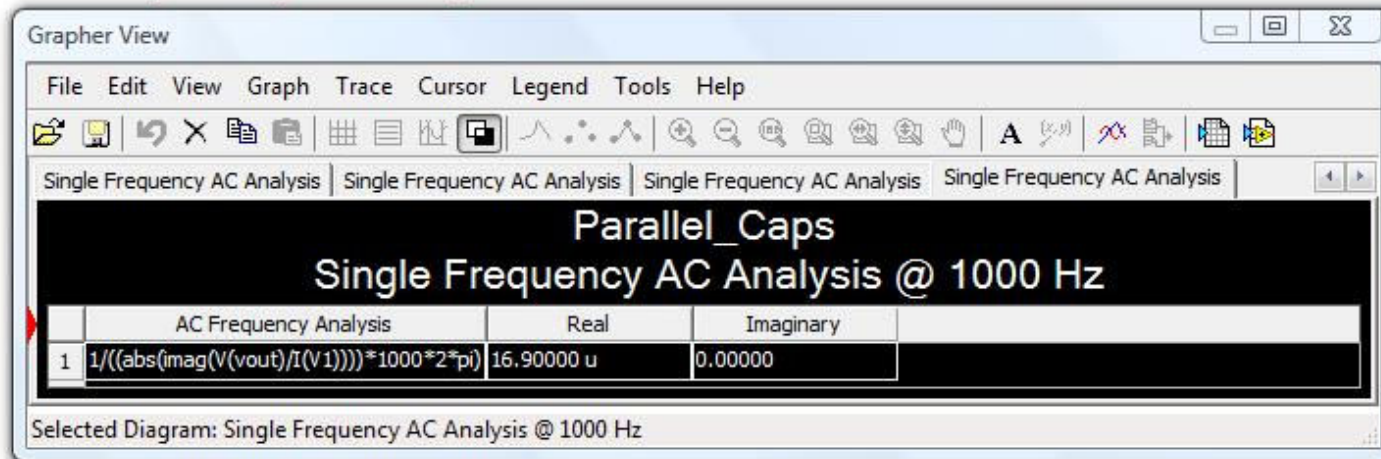The total capacitance of all capacitors in parallel is always greater than the largest capacitor value.



Capacitors in Parallel		
C1=	2.2E-6	F
C2=	4.7E-6	F
C3=	10.0E-6	F
CT=	16.900E-6	F

Combining Capacitors in Series

13


3 approaches can be taken to calculate total capacitance in series.

- For two or more capacitors of equal value $[C1 / Cn]$
(Any capacitor value / # of capacitors) can be used.
- For two capacitors of any value $[(C1 + C2) / (C1 * C2)]$
(Product of both capacitor values / sum of both capacitor values).
- For 3 or more capacitors of any value use the reciprocal of the sum of the reciprocal of all capacitor values.
 $[1 / (1 / C1) + (1 / C2) + (1 / C3) \dots]$


Capacitors of same value in Series

14

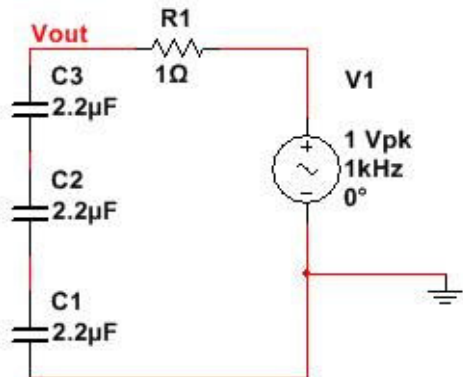Calculate total capacitance by dividing the value of one capacitor by the number of capacitors in the series circuit.





Farads=F	Anyone/Count
C1=	2.2E-6 F
C2=	2.2E-6 F
C3=	2.2E-6 F
CT=	733.333E-9 F

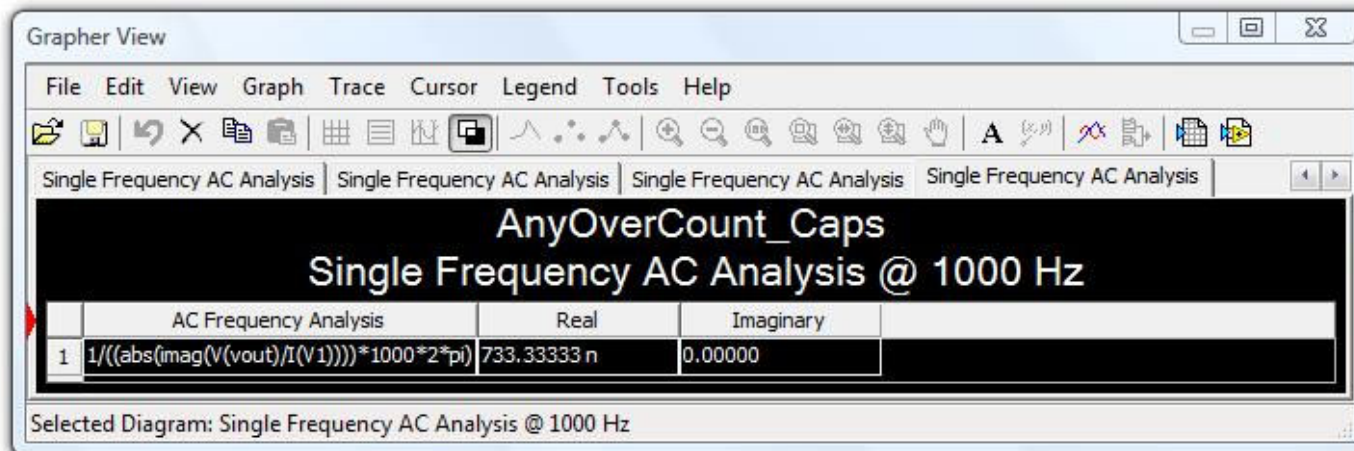

Two Capacitors of Different Values

15

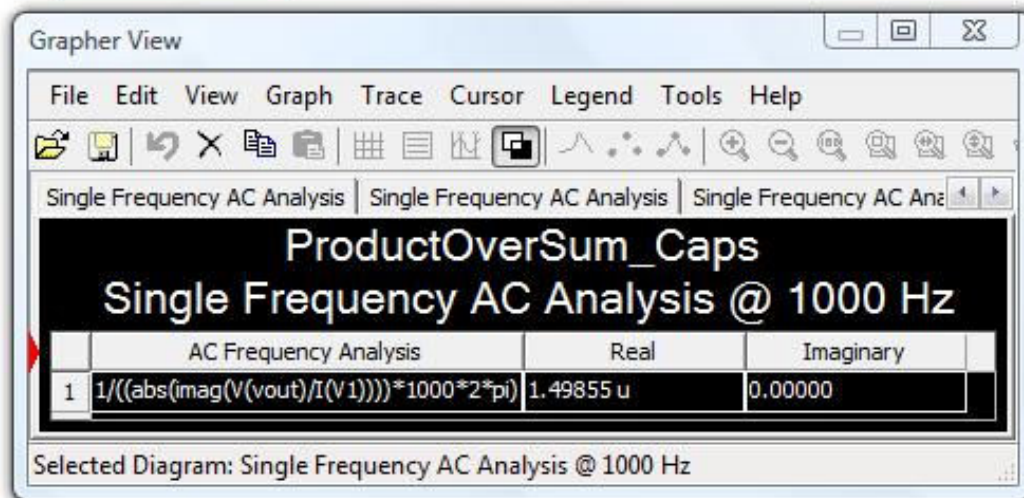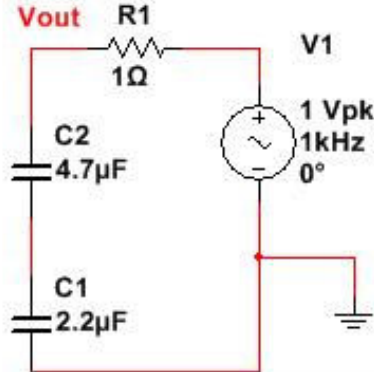To calculate two capacitors of the same or different values use the product divided by the sum method.




$(C1*C2)/(C1+C2)$		
C1=	2.2E-6	F
C2=	4.7E-6	F
CT=	1.499E-6	F


The Reciprocal of the Sum of the Reciprocal Capacitor Values

16

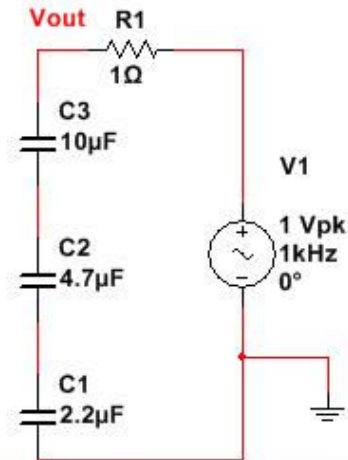This method works for calculating all series capacitor circuits.



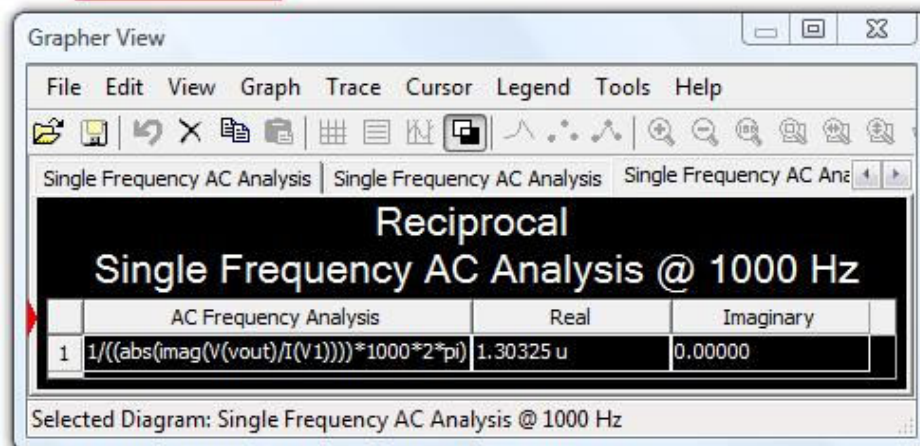The total capacity of all capacitors in series is always less than the smallest capacitor value.



1/SUM(Reciprocals of all)		
C1=	2.2E-6	F
C2=	4.7E-6	F
C3=	10.0E-6	F
CT=	1.303E-6	F

RC Time Constant

17

The RC time constant, also called tau (τ), is the time constant (in seconds) of a RC circuit.

- $\tau = R * C$
 - ▣ R = resistor's value (in Ohms)
 - ▣ C = capacitor's value (in Farads)
- The Charge and Discharge rate are inversely logarithmic and are explained in greater detail on the next slide.


$$\text{Charging } V(t) = V_0(1 - e^{-t/\tau})$$

$$\text{Discharging } V(t) = V_0(e^{-t/\tau})$$

RC Time Constant as a Function of Time.

18

As the voltage difference between the supply and the capacitor reduces, so does current. This has an inverse effect on the charge rate. This means it gets closer to 100% charged as it gets closer to infinite time. The discharge rate is just as consistent, giving us predictability. As you can see from the chart, it takes about 5 Time Constants for the capacitor to reach about 99% of full charge or about 1% from full discharge.


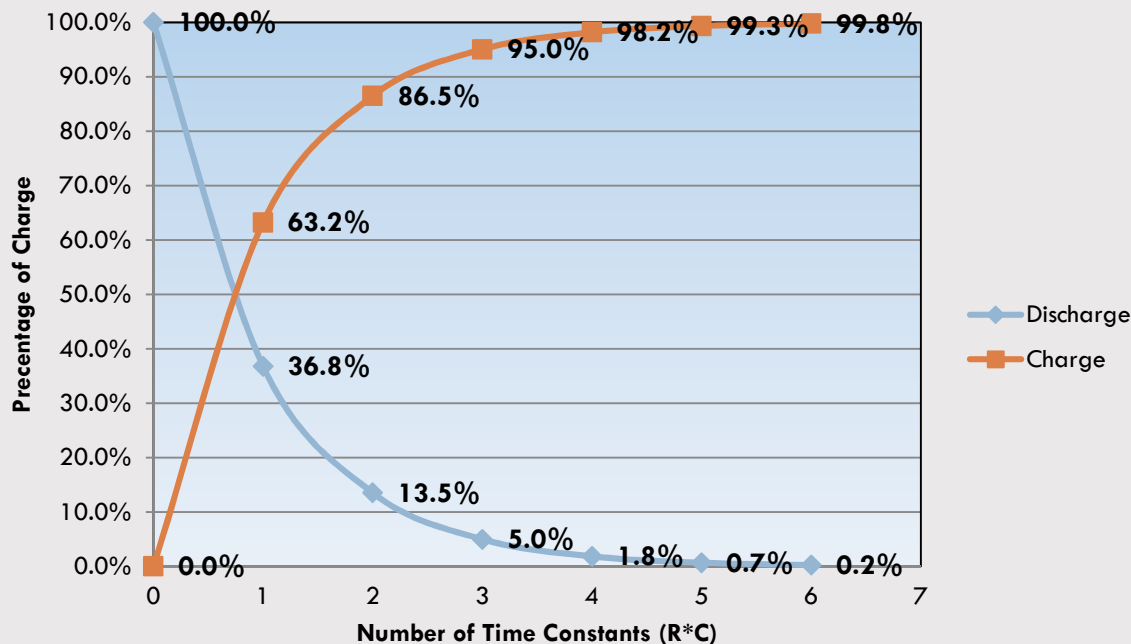


$V_S =$	1	VDC
$R =$	1.0E+3	Ω
$C =$	1.0E-3	Farads
$(R * C = \tau) \tau =$	1	
RC Time Constant		
(tc)	Discharge	Charge
0	100.0%	0.0%
1	36.8%	63.2%
2	13.5%	86.5%
3	5.0%	95.0%
4	1.8%	98.2%
5	0.7%	99.3%
6	0.2%	99.8%

RC Circuit Reaction to Pulsating VDC

19

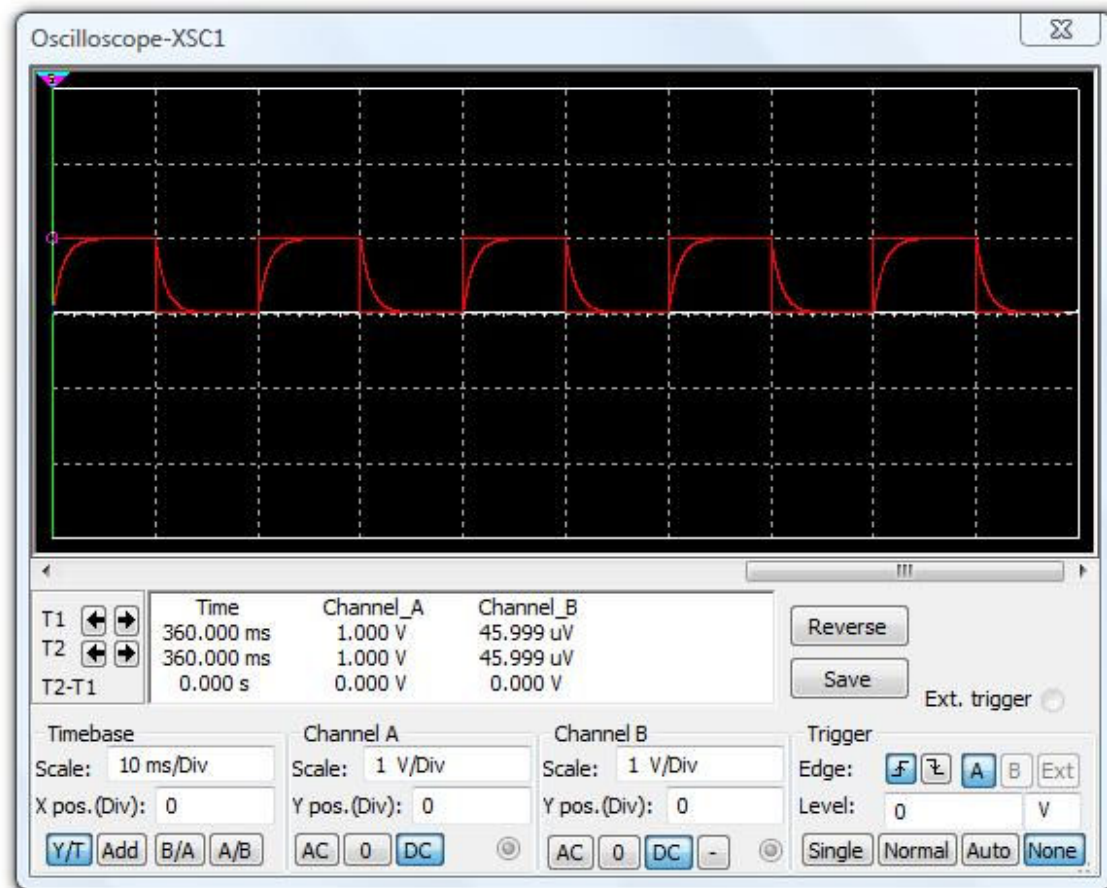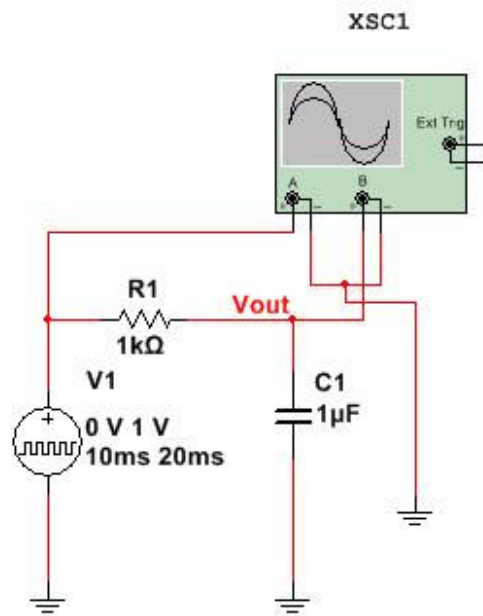The simulation curve mimics that of the calculated charge and discharge curve.



Xc at a Fixed Frequency.

20

Capacitive Reactance (X_c) is the opposition (resistance in ohms) of a charge across the capacitor. X_c is inversely proportional to frequency and capacitance within the circuit.

$$X_c = \frac{1}{2\pi fC}$$


Where,

X_c = Inductive reactance in ohms

f = Frequency in hertz

C = Capacitance in farads

$X_c = 1/(2\pi fC)$	
	R= 1000
	Input Hz= 100
Capacitance	X_c
2.0E-6	795.8E+0
4.0E-6	397.9E+0
6.0E-6	265.3E+0
8.0E-6	198.9E+0
10.0E-6	159.2E+0
12.0E-6	132.6E+0
14.0E-6	113.7E+0
16.0E-6	99.5E+0
18.0E-6	88.4E+0
20.0E-6	79.6E+0

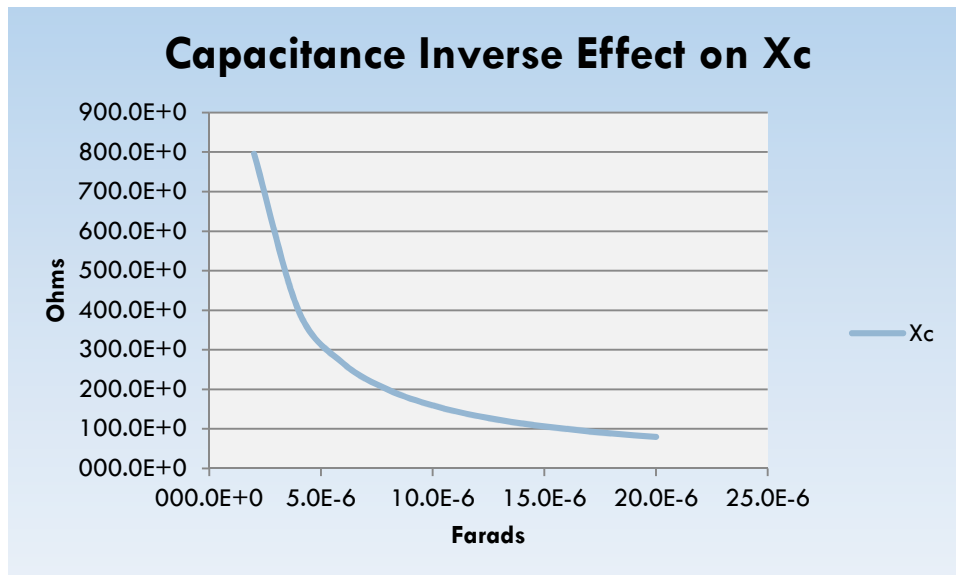


Picture Courtesy of http://www.faqs.org/docs/electric/Ref/REF_1.html

Xc Reactance of Frequency

21


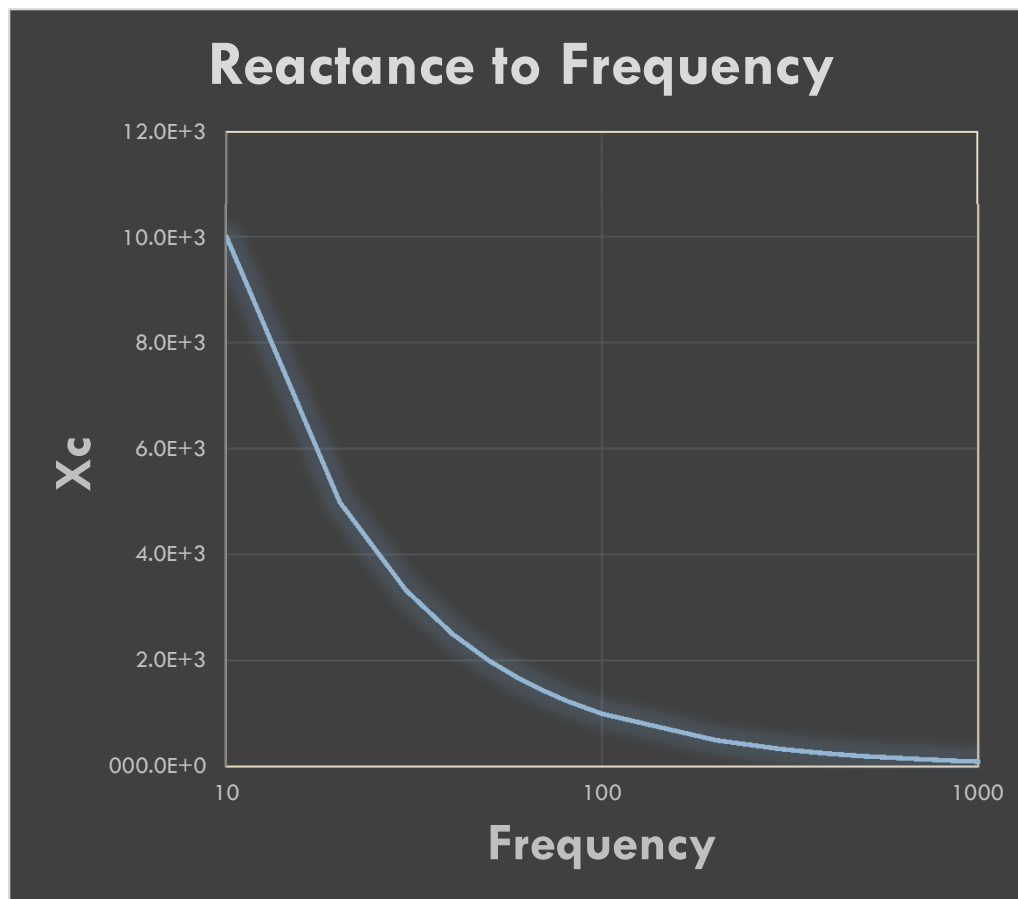
As stated in the previous slide, Xc has an inverse reaction to frequency.



Frequency	Xc for 1.59 μ F
10	10.0E+3
20	5.0E+3
30	3.3E+3
40	2.5E+3
50	2.0E+3
60	1.7E+3
70	1.4E+3
80	1.3E+3
90	1.1E+3
100	1.0E+3
200	500.0E+0
300	333.3E+0
400	250.0E+0
500	200.0E+0
600	166.7E+0
700	142.9E+0
800	125.0E+0
900	111.1E+0
1000	100.0E+0

Xc Reactance of Frequency Cont.

22

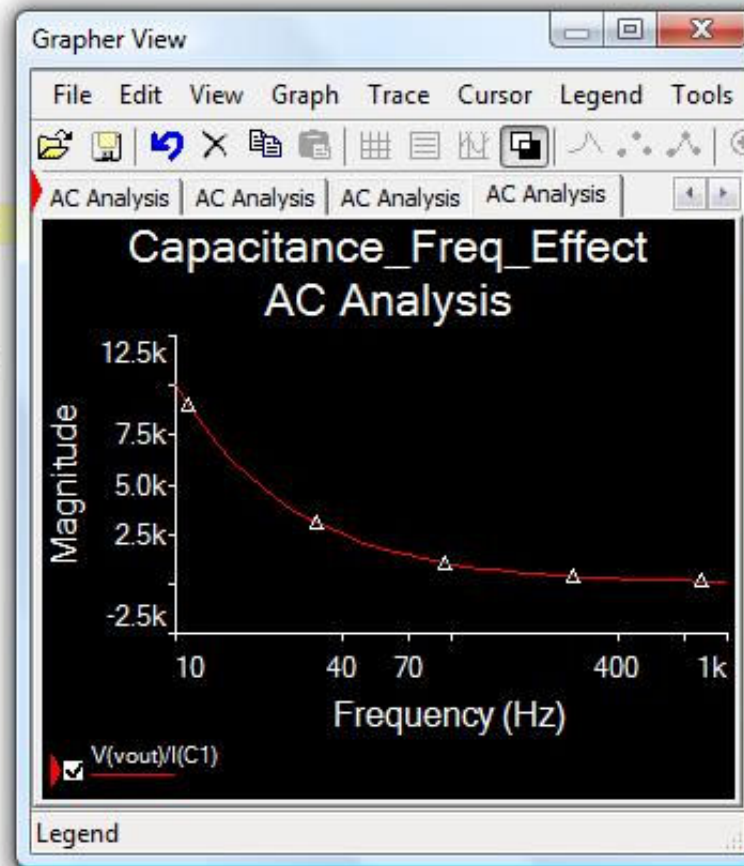
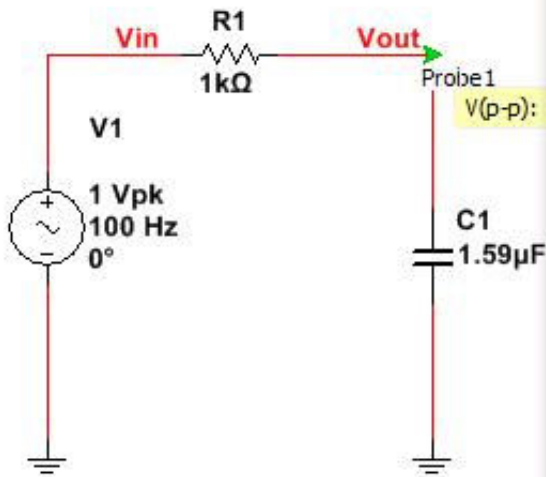


Frequency	Xc for 1.59μF
10	10.0E+3
20	5.0E+3
30	3.3E+3
40	2.5E+3
50	2.0E+3
60	1.7E+3
70	1.4E+3
80	1.3E+3
90	1.1E+3
100	1.0E+3
200	500.0E+0
300	333.3E+0
400	250.0E+0
500	200.0E+0
600	166.7E+0
700	142.9E+0
800	125.0E+0
900	111.1E+0
1000	100.0E+0

Combining Inductors in Series

23

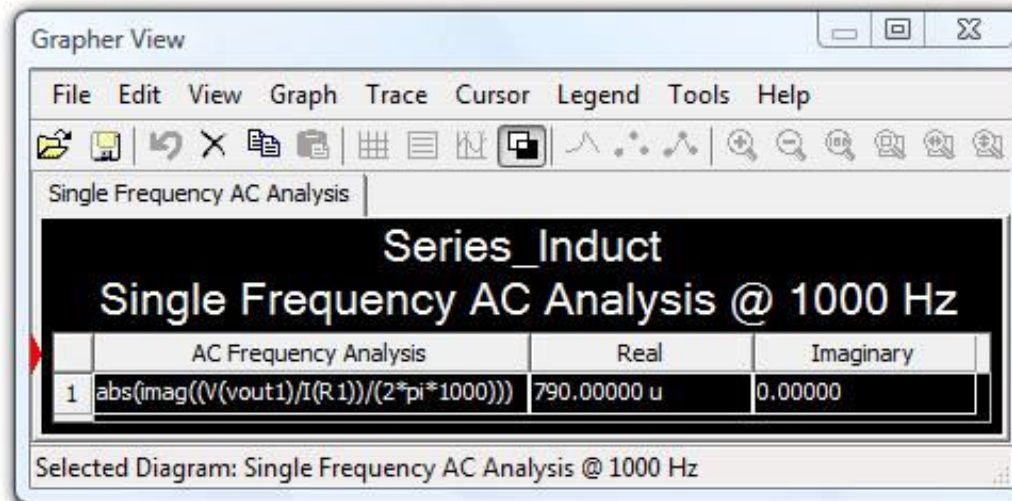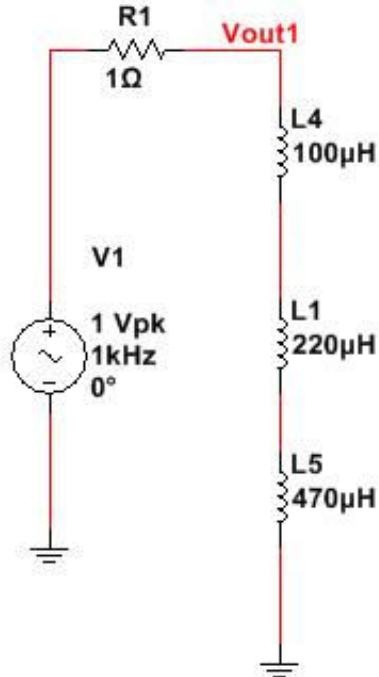The sum of all inductor values equals total inductance when in series.



LT=L1+L2+L3...	
L1=	100.0E-6
L2=	220.0E-6
L3=	470.0E-6
LT=	790.0E-6

The total inductance of all inductors in series is always greater than the largest inductor value.

Combining Inductors in Parallel

24


3 approaches can be taken to calculate total inductance in parallel.

- For two or more Inductors of equal value $[L1 / Ln]$
(Any Inductor value / # of Inductors) can be used.
- For two Inductors of any value $[(L1 + L2) / (L1 * L2)]$
(Product of both Inductor value values / sum of both Inductor value values).
- For 3 or more Inductors of any value use the reciprocal of the sum of the reciprocal of all Inductor value values.
 $[1 / (1 / L1) + (1 / L2) + (1 / L3) \dots]$


Inductors of same value in Parallel

25

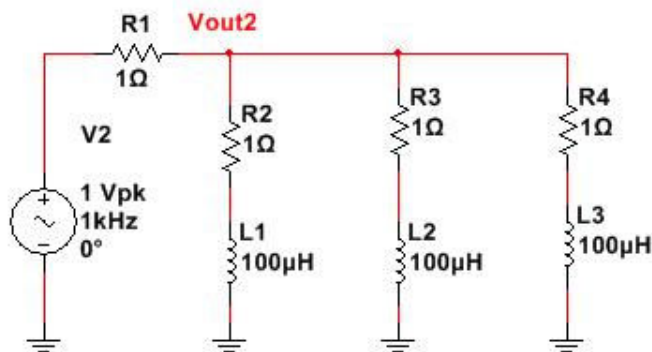Calculate total inductance by dividing the value of one inductor by the number of inductors in the parallel circuit.



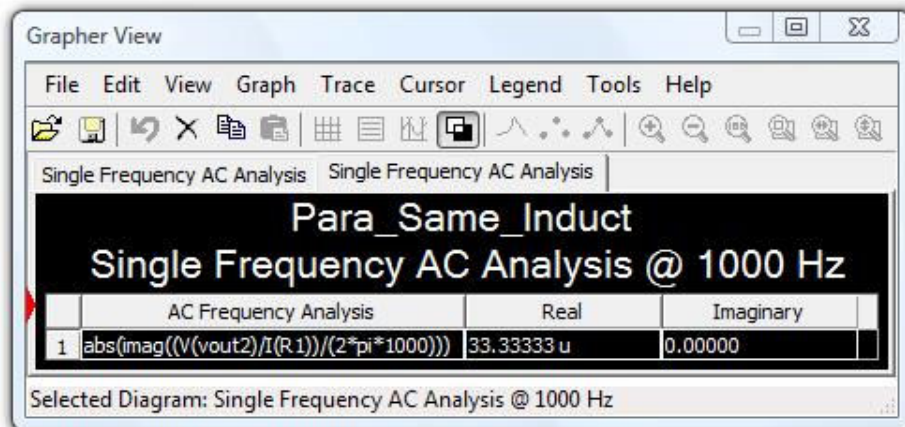The total inductance of all inductors in series is always less than the smallest inductor value.





$LT = \text{Any}L / \text{Count}L$	
L1=	100.0E-6
L2=	100.0E-6
L3=	100.0E-6
LT=	33.3E-6

Two Inductors of Different Values

26

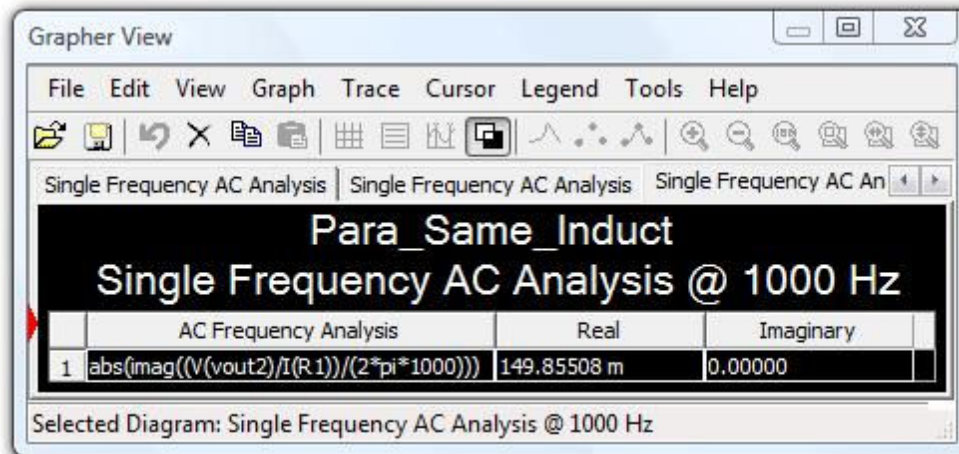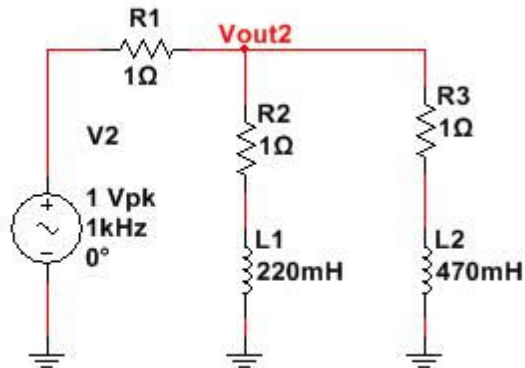To calculate two inductors of the same or different values within a parallel circuit use the product divided by the sum method.




$LT=(L1*L2)/(L1+L2)$	
L1=	220.0E-3
L2=	470.0E-3
LT=	149.9E-3

The Reciprocal of the Sum of the Reciprocal Inductors Values

27

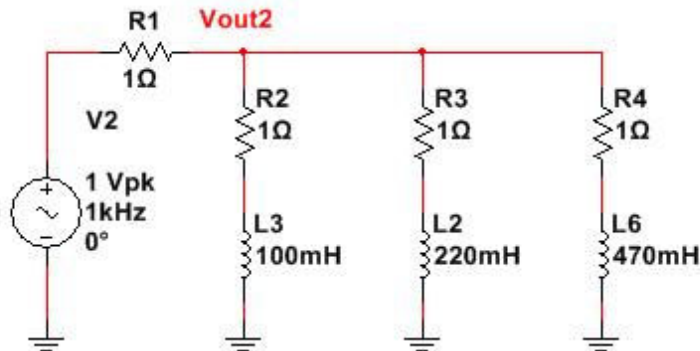This method works for calculating all parallel inductor circuits




$$L_T = 1 / ((1/L_1) + (1/L_2) + (1/L_3) \dots)$$

$$L_1 = 100.0E-3$$

$$L_2 = 220.0E-3$$

$$L_3 = 470.0E-3$$

$$L_T = 59.98E-3$$

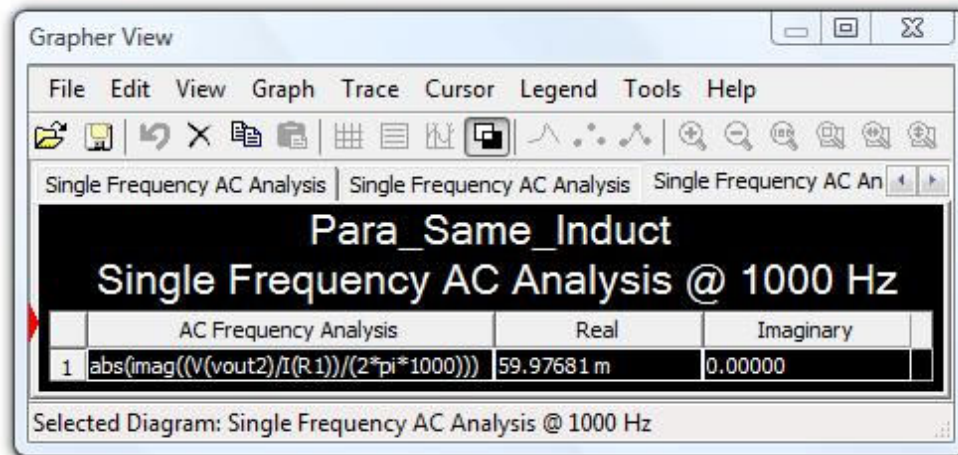

RL Time Constant

28

The RL time constant, also called tau (τ), is the time constant (in seconds) of a RL circuit.


- $\tau = L/R$
 - ▣ R = resistor's value (in Ohms)
 - ▣ L = Inductor's value (in Henrys)
- The Charge and Discharge rate are inversely logarithmic and are explained in greater detail on the next slide.

$$\text{Charging } V(t) = V_0(1 - e^{-t/\tau})$$

$$\text{Discharging } V(t) = V_0(e^{-t/\tau})$$

RL Time Constant as a Function of Time.

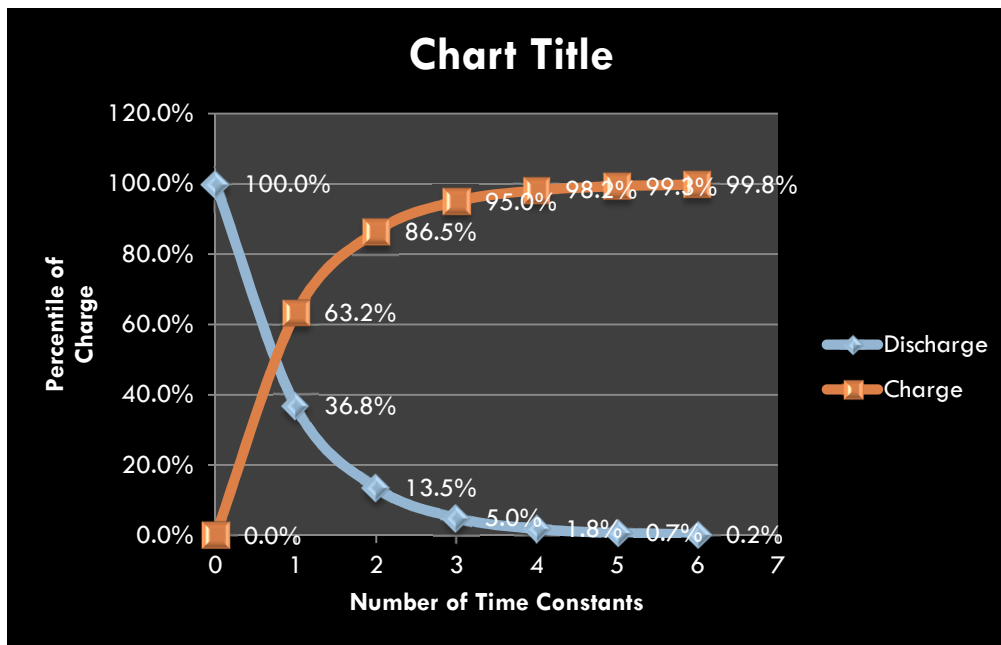An inductor is similar to a capacitor as it stores a charge but has a different approach. An inductor stores the charge in an electrical magnetic field (EMF) around its coil and in a core if present. As the current flows through the coil a back EMF (CEMF) is generated that opposes the charge. This gives an inverse charge-rate and discharge-rate, like a capacitor it will never reach 100% or 0%.





$V_r = V_s * (e^{-t/\tau}) / V_r = V_s * (1 - e^{-t/\tau})$		
Vs=	1	VDC
R=	1.0E+3	Ω
L=	1.0E+3	Henrys
(L/R= τ) τ =	1.0E+0	
RL Time Constant		
(tc)	Discharge	Charge
0	100.0%	0.0%
1	36.8%	63.2%
2	13.5%	86.5%
3	5.0%	95.0%
4	1.8%	98.2%
5	0.7%	99.3%
6	0.2%	99.8%

RL Circuit Reaction to Pulsating VDC

30

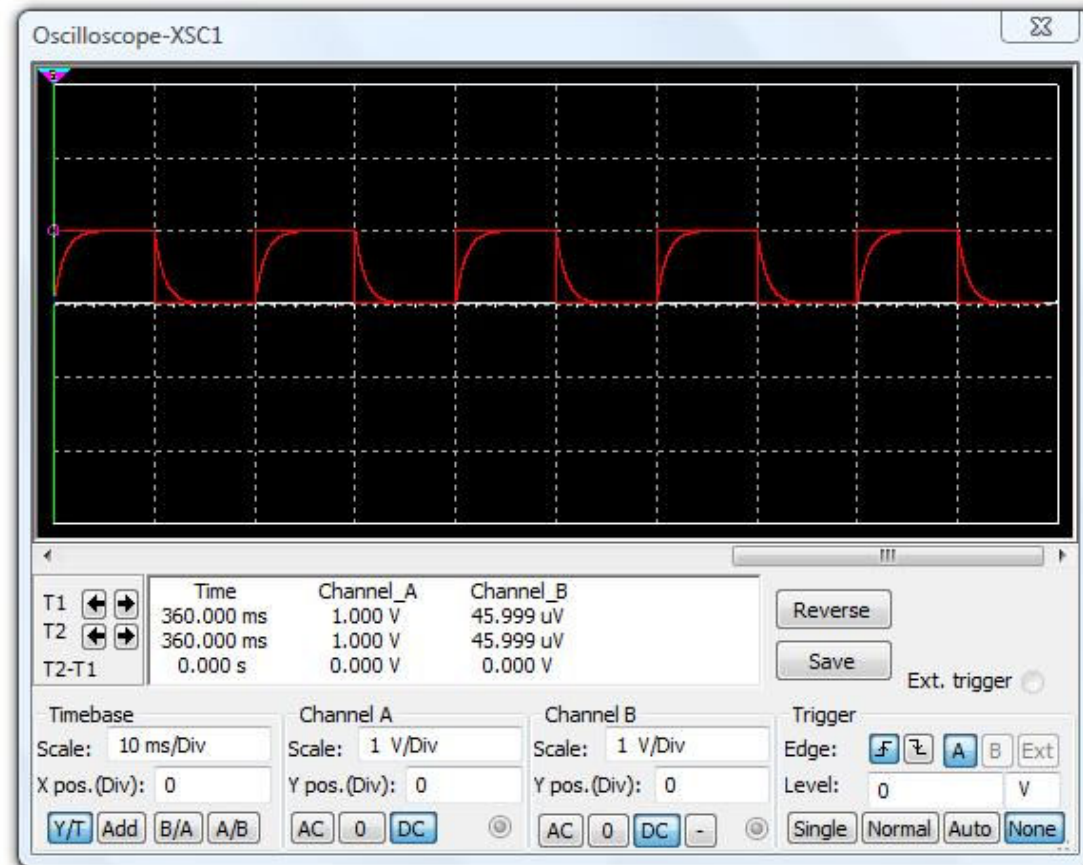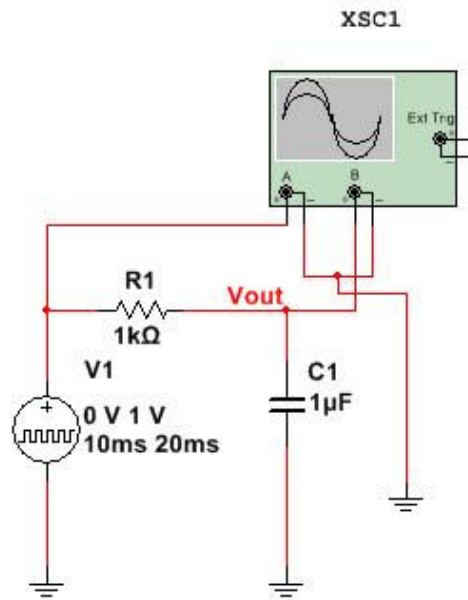The simulation curve mimics that of the calculated charge and discharge curve.



XI at a Fixed Frequency.

31

Inductive Reactance (XI) is the opposition (resistance) of a charge across the inductor. XI is linear proportional to frequency and inductance within the circuit.

$$X_L = 2\pi fL$$


Where:

X_L = the inductive reactance in ohms

f = the frequency in hertz

L = the inductance in henrys

$\pi = 3.1416$

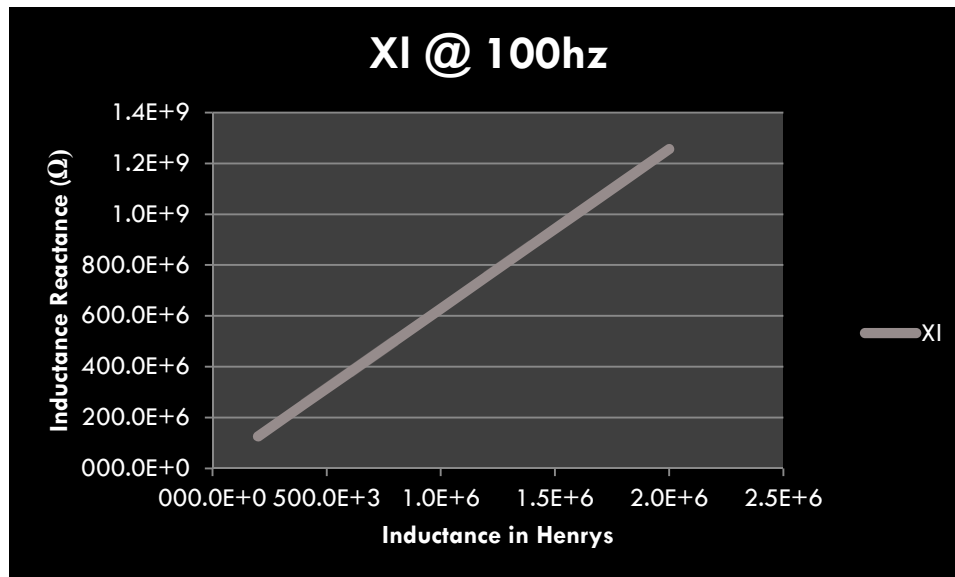


XI=2πfL	
R=	1000
Input Hz=	100
Inductance	XI
200.0E+3	125.7E+6
400.0E+3	251.3E+6
600.0E+3	377.0E+6
800.0E+3	502.7E+6
1.0E+6	628.3E+6
1.2E+6	754.0E+6
1.4E+6	879.6E+6
1.6E+6	1.0E+9
1.8E+6	1.1E+9
2.0E+6	1.3E+9

Picture Courtesy of <http://www.tpub.com/neets/book9/34a.htm>

XI Reactance to Frequency

32

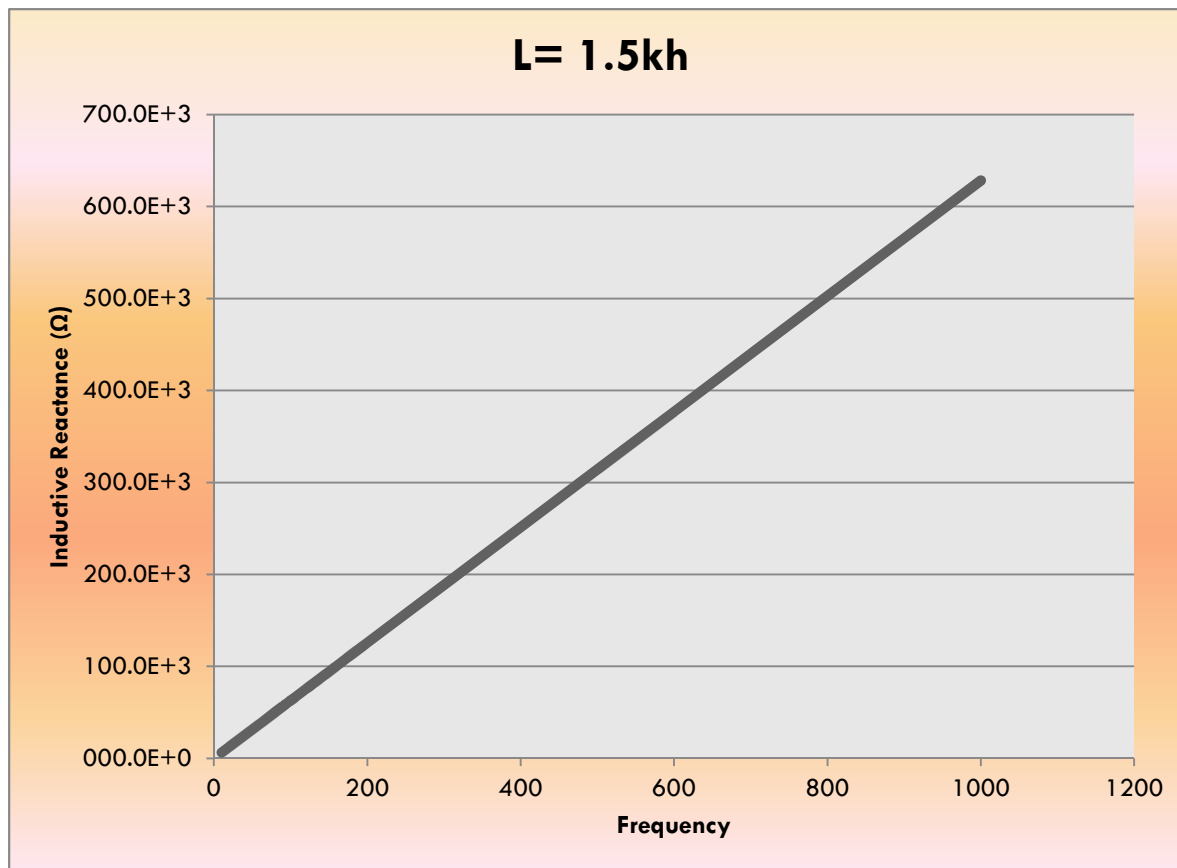As stated in the Previous Slide, XI has a linear Reaction to Frequency.



Va= 1	R= 1k Ω
Frequency	L= 1.5kh
10	6.3E+3
20	12.6E+3
30	18.8E+3
40	25.1E+3
50	31.4E+3
60	37.7E+3
70	44.0E+3
80	50.3E+3
90	56.5E+3
100	62.8E+3
200	125.7E+3
300	188.5E+3
400	251.3E+3
500	314.2E+3
600	377.0E+3
700	439.8E+3
800	502.7E+3
900	565.5E+3
1.0E+3	628.3E+3