
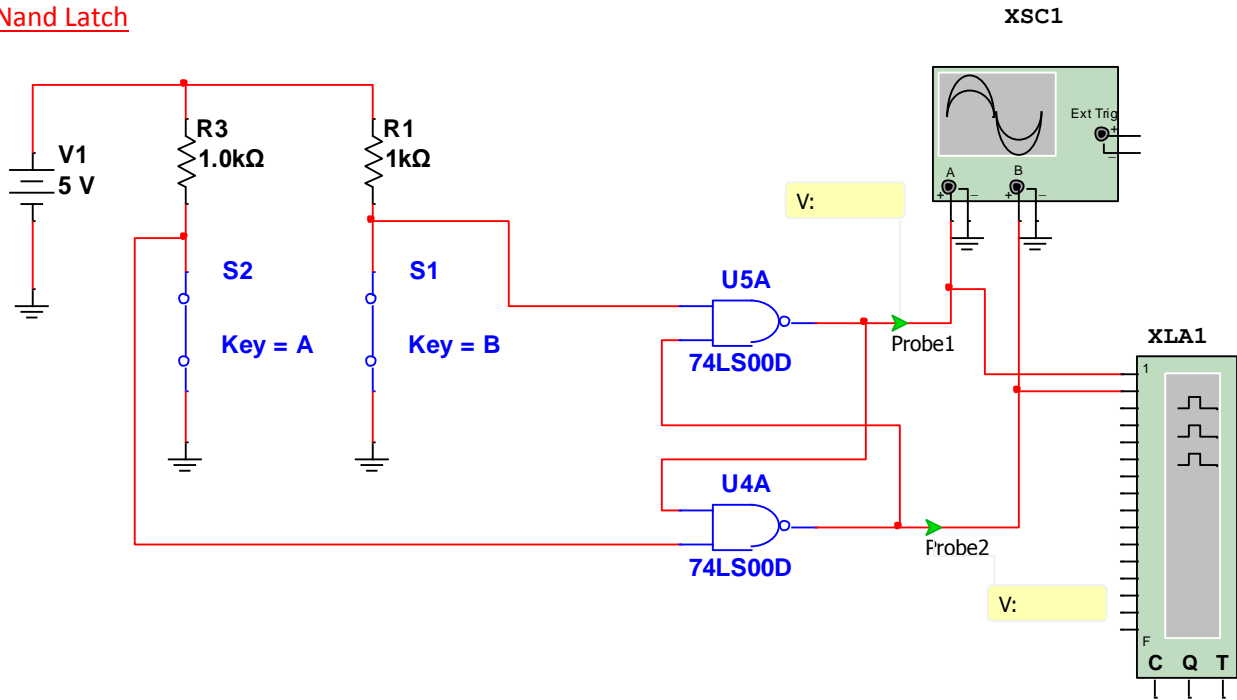


LAB 3


Nand Latch

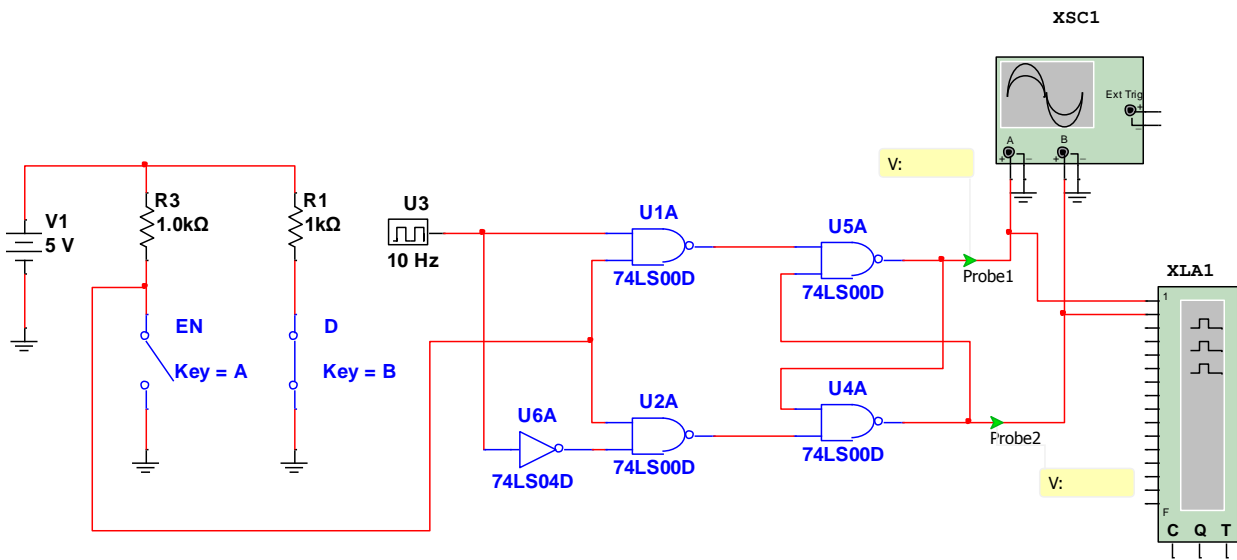



Lab 3 DFF 2





Lab 3 DFF 1

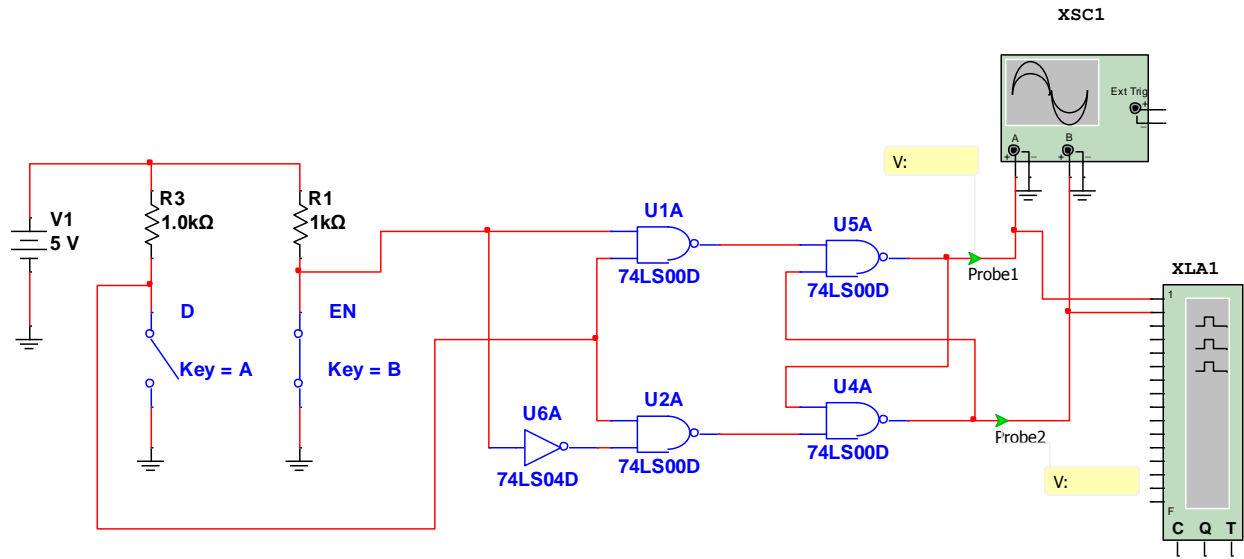



LAB 1

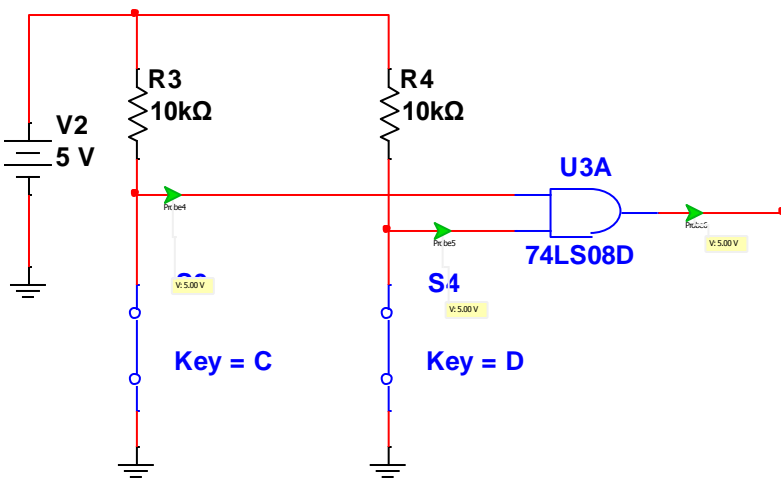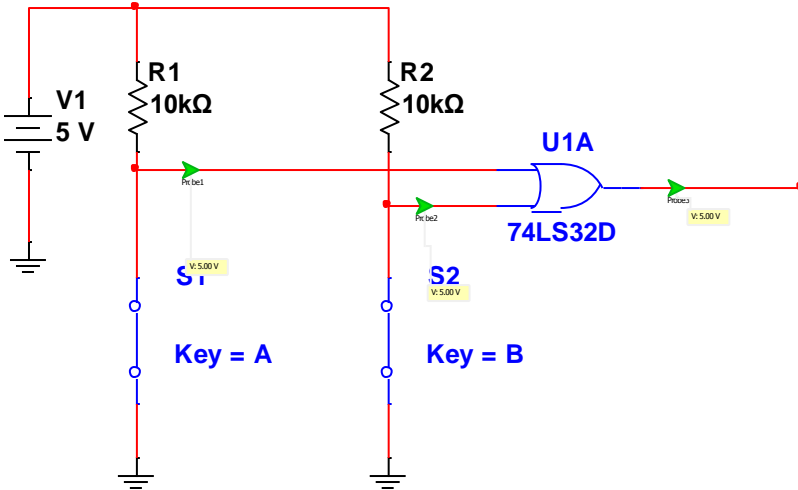

Lab 2 part A

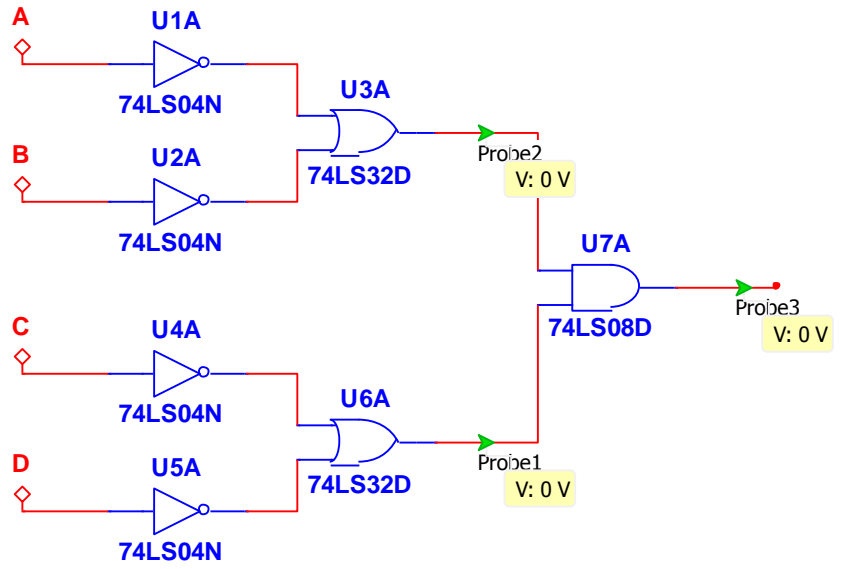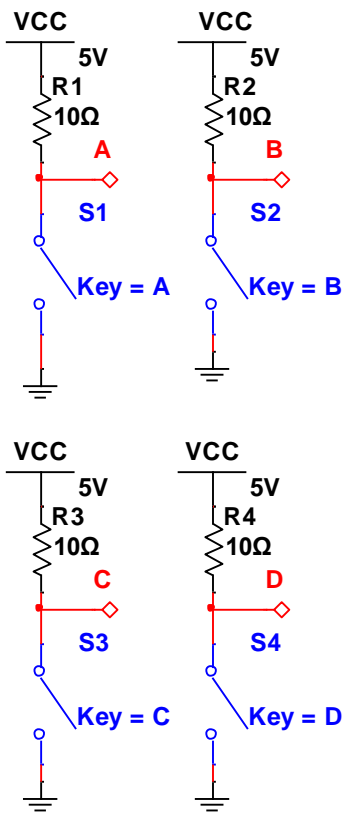

Lab 2 part b

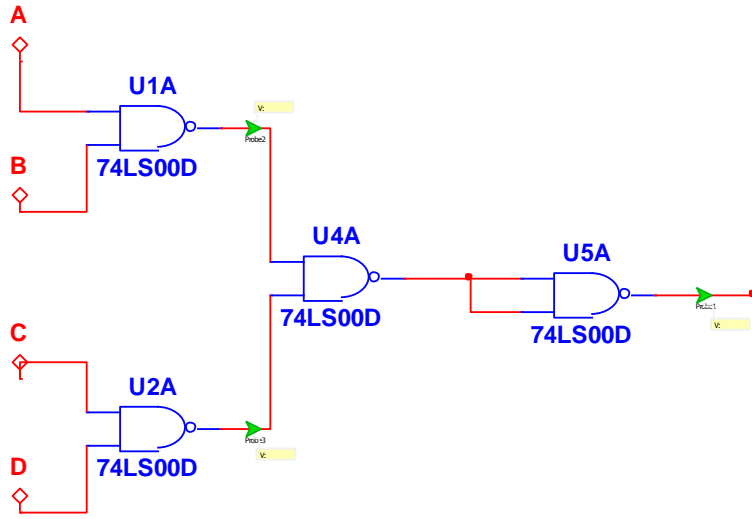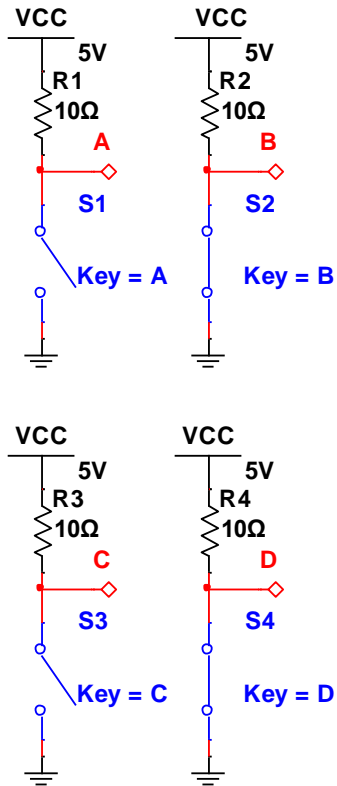

Week 13 asynchronous counters

